



CMOS Analog IC Design

Lab 5

Simple vs Wide Swing Cascode Current Mirror

Supervised by: Dr. Hesham Omran

Part 1: Exploring Sizing Tradeoffs Using SA

We want to design a simple current mirror

Sinking current means which device type? NMOS or PMOS?

Nmos

The % Change in current translates to a spec on the $\lambda = 1/V_A$ of the device. How much is the required λ ?

$$\frac{\Delta I_{out}}{I_{out}} \leq 0.1$$

$$I_D = I_{D0}(1 + \lambda V_{DS})$$

$$\frac{\Delta I_{out}}{I_{out}} \approx \lambda \cdot \Delta V_{DS}$$

$\Delta V_{DS} = 1 \text{ V}$ Then

$$\lambda \cdot 1 \leq 0.1 \Rightarrow \lambda \leq 0.1$$

From the model file, calculate σ_{VT} (var_vth at WxL = 1 μ m²) and compare it to the value in ADT. Which one is higher, why?

 


Figure 1 : Simulation of VGMIS vs. VGS for an NMOS transistor with W/L = 1u/1u

+ par_vth=0.007148

simulated Value

From the graph above, the value of VGMIS ranges between 4.9mV and 6.0mV. The measured value at VGS = 500mV is **5.131mV**.

2. Theoretical Value

The theoretical value is calculated using the formula from the model file (sm141064.ngspice):

Where:

- par_vth = 0.007148
- For W = 1 μ m and L = 1 μ m \rightarrow area = 1 μ m² \rightarrow p_sqrtarea = $\sqrt{(1e-12)} = 1e-6$

So:

$$\text{var}_{vth} = \frac{0.7071 \times 0.007148 \times 1e-6}{1e-6} = 0.7071 \times 0.007148 = \mathbf{5.23 \text{ mV}}$$

3. Comparison and Comment

- Simulated VGMIS (from ADT) \approx 5.131 mV
- Theoretical var_vth (from model) \approx 5.23 mV

Comment: This close agreement between the results confirms that the simulation model used in the ADT tool (the Look-Up Table or LUT) accurately reflects the theoretical mathematical model of the transistor. This provides confidence in the tool's results for subsequent design steps.

Plot L, W, AREA, and λ . The results will not be smooth due to the bumpy mismatch data in the LUT.

And The final design point was selected at $V^* = 150$ mV to meet the compliance voltage constraint. At this point, the estimated mismatch in output current was:

 


Figure 2 : Required transistor width (W) versus Overdrive Voltage (V^*) for a constant output current mismatch. The cursor indicates the value at $V^* = 150$ mV.

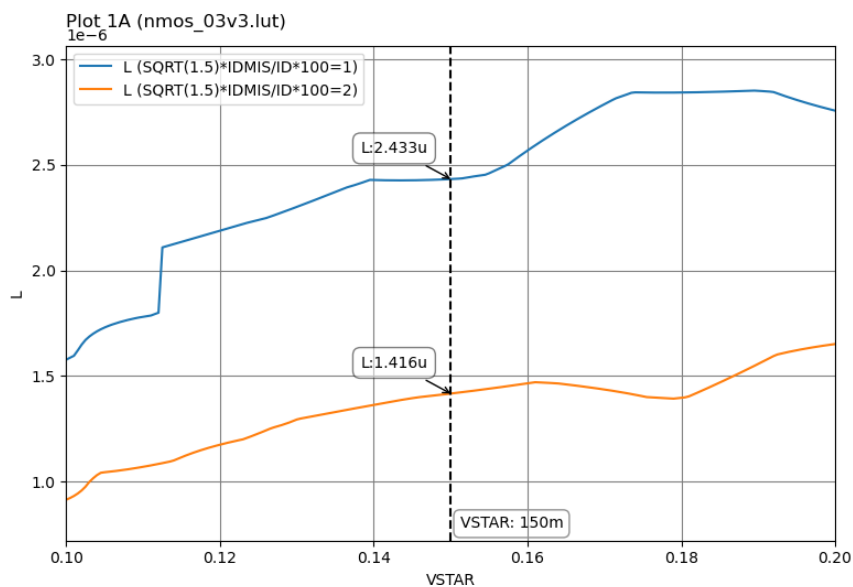


Figure 3 : Required transistor length (L) versus Overdrive Voltage (V^*) for a constant output current mismatch. The cursor indicates the value at $V^* = 150$ mV.

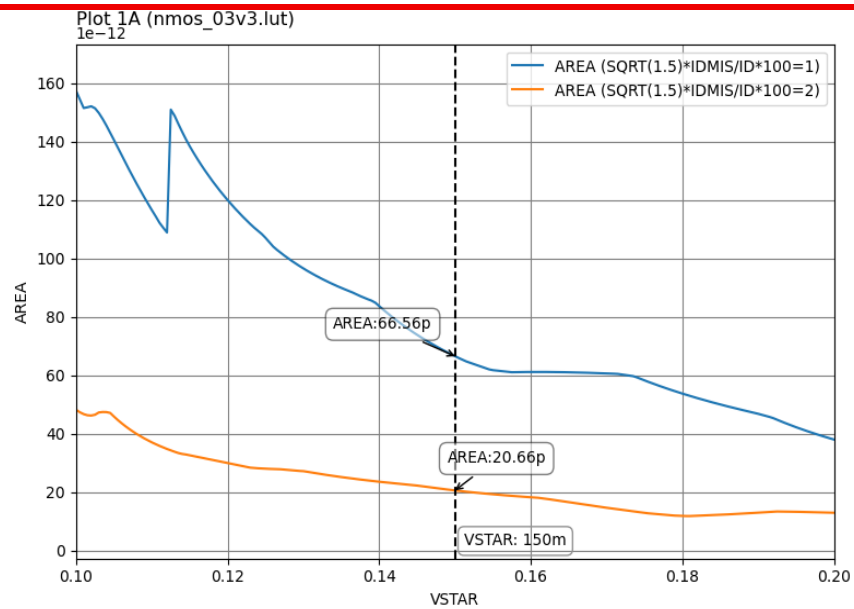


Figure 4 : Resulting device area ($W \times L$) versus Overdrive Voltage (V^*) for a constant output current mismatch. The cursor indicates the value at $V^* = 150\text{mV}$.

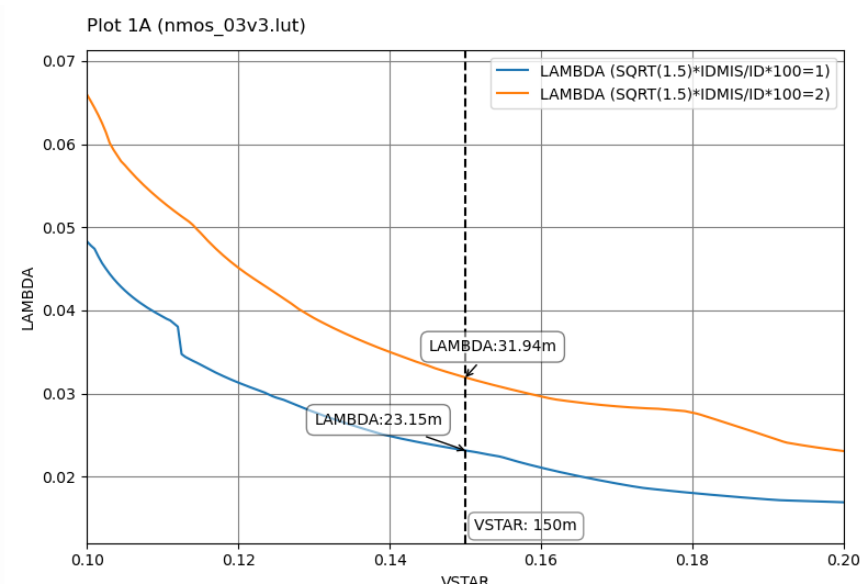


Figure 5 : Channel length modulation parameter (λ) versus Overdrive Voltage (V^*) for a constant output current mismatch. The cursor indicates the value at $V^* = 150\text{mV}$, which must be checked against the design specification.

At fig 5 the two graph have $\lambda < 0.1$


We will use the minimum Area then

From fig 2,3

$W = 14.58\text{ }\mu\text{m}$

$L = 1.416\text{ }\mu\text{m}$

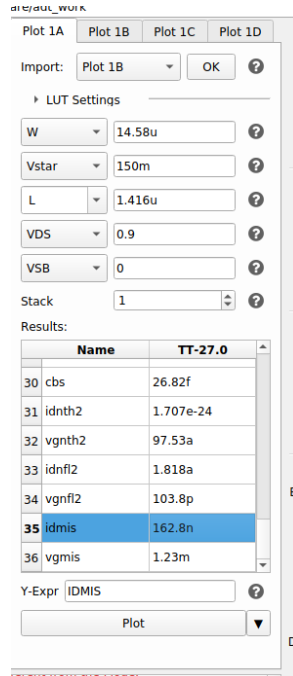After we chose W and L we will calculate Idmis



Plot 1A Plot 1B Plot 1C Plot 1D

Import: Plot 1B OK ?

LUT Settings

W 14.58u ?

Vstar 150m ?

L 1.416u ?

VDS 0.9 ?

VSB 0 ?

Stack 1 ?

Results:

Name	TT-27.0
30 cbs	26.82f
31 idnth2	1.707e-24
32 vgnth2	97.53a
33 idnfl2	1.818a
34 vgnfl2	103.8p
35 idmis	162.8n
36 vgmis	1.23m

Y-Expr IDMIS ?

Plot

Idmis = 162.8n

Report the device sizing and $\sigma(I_{out})/I_{out}$ at the selected design point

$$\frac{\sigma(I_{out})}{I_{out}} = \sqrt{1 + \frac{1}{m} \cdot \frac{idmis}{I_D}} \cdot 100$$

m = 2

$$\frac{\sigma(I_{out})}{I_{out}} = \sqrt{1 + \frac{1}{2} \cdot \frac{162.8 \times 10^{-9}}{10 \times 10^{-6}}} \cdot 100 = \sqrt{1.5} \cdot 0.01628 \cdot 100$$

$$= 1.225 \cdot 1.628\% = \boxed{1.996\%}$$

The final design was chosen at $V = 150 \text{ mV}^*$ to meet the compliance voltage requirement.

At this point, the output current mismatch was calculated as $\sigma(I_{out})/I_{out} \approx 1.996\%$, which satisfies the 2% limit.

This part focuses on designing and simulating simple and wide-swing current mirrors. It evaluates their performance through DC analysis, compliance voltage, and mismatch behavior.

@m.xm6.m0[vds]
0.2009

0.22
0.20076
0.18
0.16

22k 24k 26k 28k 30k

res-sweep 27.208k

RB=27.2K

OP Annotation :

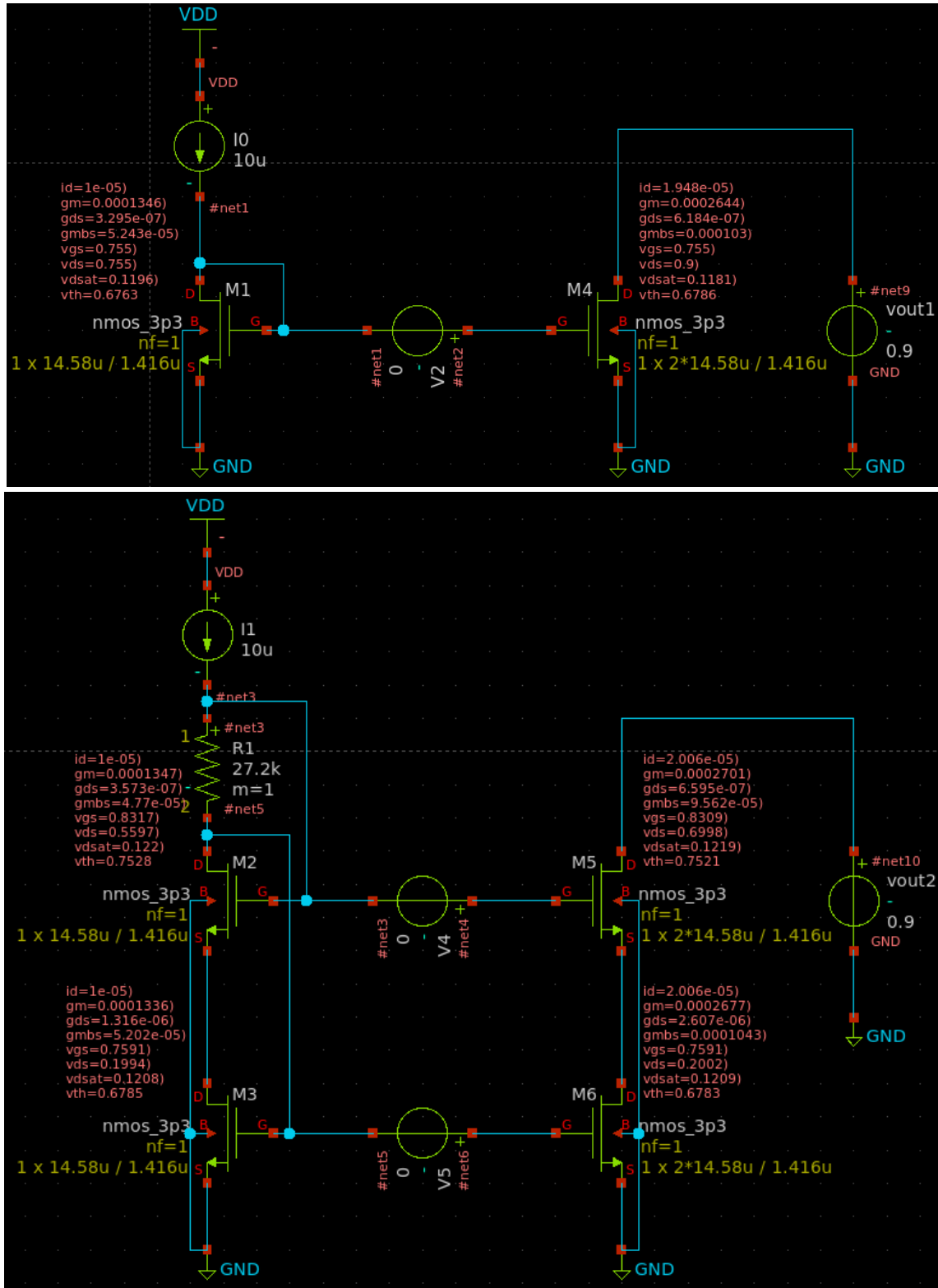


Figure 8 : Operating point (OP) analysis results for the wide-swing cascode current mirror using the selected R_B , confirming all transistors are in saturation.

All Transistors in Saturation $V_{ds} > V_{dsat}$ and

DC Sweep (I_{out} vs V_{OUT})

This section analyzes how I_{out} changes with V_{out} for both current mirror types.

We determine compliance voltage, percent error, and plot output resistance (R_{out}) over the mirror's operating range.

 


Figure 9 : Comparison of the output current (I_{out}) versus output voltage (V_{OUT}) for the simple and wide-swing cascode current mirrors.

Comment on the difference:

The wide-swing current mirror reaches its constant output current at a much lower output voltage compared to the simple mirror. This shows that the wide-swing design has a better (lower) compliance voltage. The simple mirror needs a higher V_{OUT} to maintain saturation in the output transistor.

Estimated compliance voltages:

- **Wide-swing mirror:** Compliance voltage is approximately 0.24 V.
- **Simple mirror:** Compliance voltage is around 0.135 V.

I_{out} of the simple CM is exactly equal to $I_B \cdot 2$ at a specific value of V_{OUT} . Why?

- I_{out} equals $I_B \cdot 2$ only when the (V_{DS}) of the input and output transistors match exactly.
- At this point, channel length modulation effects cancel out, resulting in perfect current mirroring.

For the simple current mirror, calculate the percent change in I_{out} when V_{OUT} changes from 0.5V to 1.5V (i.e., 1V change). Compare the result to the value expected from Part 1.

$I_{out} \text{ (at } V_{out} = 0.5) = 20.1 \mu A$

$I_{out} \text{ (at } V_{out} = 1.5) = 20.8 \mu A$

The change in current is:

$$\Delta I_{out} = I_2 - I_1 = 20.8 \mu A - 20.1 \mu A = 0.7 \mu A$$

The percent change is calculated relative to the initial current:

$$\text{Percent Change} = \frac{\Delta I_{out}}{I_1} \times 100 = \frac{0.7 \mu A}{20.1 \mu A} \times 100 \approx 3.48\%$$

Comparison

- **Calculated Result: 3.48%**
- **Expected Result from Part 1: The design specification required the change to be < 10%.**

The calculated change of 3.48% is well within the required specification, confirming a successful design that significantly outperforms the initial target.

 


Figure 10 : Percent error in output current versus output voltage for both current mirrors.

- The **wide-swing CM** (cyan curve) reaches a very small error percentage at a low voltage (around 0.3V) and maintains that high accuracy as the output voltage increases.
- The **simple CM** (red curve), in contrast, shows an error that continuously changes with the output voltage. It only crosses the zero-error point at one specific voltage (around 1.2V) and is less accurate everywhere else.

 


Figure 11 : Comparison of the output resistance (R_{out}) versus output voltage (V_{OUT}) on a logarithmic scale.

Comment on the difference between the two circuits.

The primary difference observed in the R_{out} versus V_{OUT} plot is that the **wide-swing current mirror** exhibits a significantly higher output resistance compared to the simple current mirror within the operating region.

- The **wide-swing mirror** achieves an output resistance in the range of hundreds of mega-ohms, behaving almost like an ideal current source.
- In contrast, the **simple mirror**, despite having some resistance due to the basic cascode structure, stabilizes at a much lower value
- As a result, the wide-swing circuit is far more effective at rejecting variations in output

Does R_{out} change with V_{OUT} ? Why?

Yes, the output resistance (R_{out}) changes with the output voltage (V_{OUT}) for both circuits.

- **At low V_{OUT} :** The output transistors are in the **triode region**, where they behave more like low-value resistors. This is why R_{out} is low for both circuits when V_{OUT} is near zero.
- **As V_{OUT} increases:** The transistors enter the **saturation region**. The intrinsic resistance (r_o) of a MOSFET increases with its drain-source voltage (V_{DS}). Since the overall output resistance of the cascode stage depends on the intrinsic resistances of its transistors, R_{out} rises as V_{OUT} increases, eventually stabilizing once the devices are deep in saturation.

From OP

Transistor	gm (S)	ro (Ohms)	gmb (S)
M4	269.03 μ S	1.589 M Ω	104.83 μ S
M5	271.77 μ S	1.507 M Ω	96.28 μ S
M6	269.34 μ S	368.0 k Ω	104.90 μ S

Rout for simple CM = ro4 = 1.589 M Ω

Rout for Wide Swing CM = ro5(1+(gm5+gmb5)(ro6(1+(gm6+gmb6))))=205.69 M Ω

Circuit Type	Analytical Result	Simulation Result
Simple CM	1.589 M Ω	1.589 M Ω
Wide-Swing CM	205.69 M Ω	205.9 M Ω

Mismatch :

This section investigates how device mismatch impacts the output current. You'll manually introduce small mismatch voltages to see which transistors are most sensitive, providing insight into which devices need to be designed more carefully.

$$V_{max} = \frac{\sqrt{1.5 \times 3.5mV}}{\sqrt{W \times L \times 10^{12}}}$$

$V_{max} = 0.94mV$ so we will sweep from 0 to 0.94mV

For Sample CM:

 


Figure 12 : Sweep of VMIS1 applied to mirror transistor M4 to simulate threshold voltage mismatch. The plot shows the resulting deviation in output current (I_{out}).

Initial Current: 20.5uA

Final Current: 20.7uA

The change in current is:

$$\Delta I_{out} = I_{final} - I_{initial} = 20.7\mu A - 20.5\mu A = 0.2\mu A$$

The percent change is calculated relative to the initial current:

$$\text{Percent Change} = \frac{\Delta I_{out}}{I_{initial}} \times 100 = \frac{0.2\mu A}{20.5\mu A} \times 100 \approx 0.98\%$$

Analytically :

$$\Delta I_{out} = g_{m4} \cdot V_{MIS1} = 269.03 \mu S \cdot 0.94 \text{ mV} = 0.253 \mu A$$

$$\text{Percent Change} = \frac{\Delta I_{out}}{I_{out}} \times 100 = \frac{0.253 \mu A}{20.5 \mu A} \times 100 \approx \mathbf{1.23\%}$$

Comparison

- **Analytical Result: 1.23%**
- **Simulation Result: 0.98%**

For Wide Swing CM:

 


Figure 13 : Sweep of V_{MIS1} applied to mirror transistor M6 to simulate threshold voltage mismatch. The plot shows the resulting deviation in output current (I_{out}).

Initial Current: 19.9 μA

Final Current: 20.1 μA

The change in current is:

$$\Delta I_{out} = I_{final} - I_{initial} = 20.1 \mu A - 19.9 \mu A = 0.2 \mu A$$

The percent change is calculated relative to the initial current:

$$\text{Percent Change} = \frac{\Delta I_{out}}{I_{initial}} \times 100 = \frac{0.2 \mu A}{19.9 \mu A} \times 100 \approx \mathbf{1.01\%}$$

Analytically :

$$\Delta I_{out} = g_{m6} \cdot V_{MIS1} = 0.253 \mu A$$

$$\text{Percent Change} = \frac{\Delta I_{out}}{I_{out}} \times 100 = \frac{2.53 \times 10^{-7} A}{20.24 \times 10^{-6} A} \times 100 \approx 1.25\%$$

Comparison

- **Analytical Result: 1.25%**
- **Simulation Result: 1.01%**

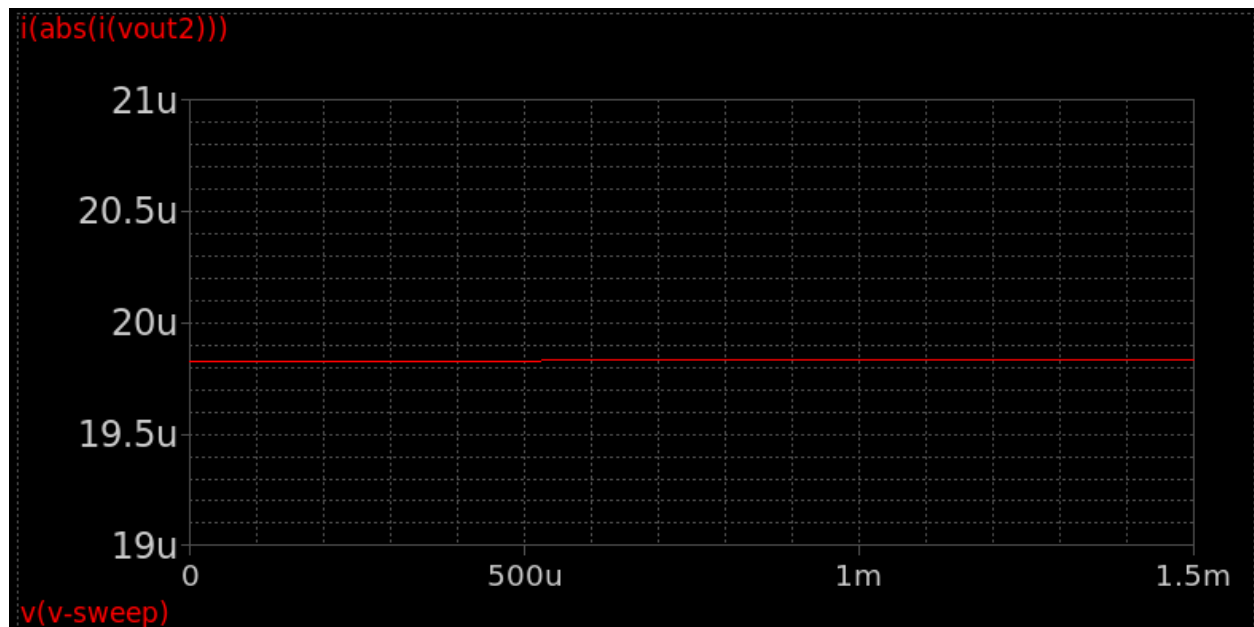


Figure 14 :: Sweep of V_{MIS2} applied to mirror transistor $M5$ to simulate threshold voltage mismatch. The plot shows the resulting deviation in output current (I_{out}).

Initial Current: $19.829 \mu A$

Final Current: $19.832 \mu A$

The change in current is:

$$\Delta I_{out} = I_{final} - I_{initial} = 19.832 \mu A - 19.829 \mu A = 0.003 \mu A \text{ (or 3 nA)}$$

The percent change is calculated relative to the initial current:


$$\text{Percent Change} = \frac{\Delta I_{out}}{I_{initial}} \times 100 = \frac{0.003 \mu A}{19.829 \mu A} \times 100 \approx 0.015\%$$

Analytically :

$$\Delta I_{out} = \frac{g_{m5}}{1 + (g_{m5} + g_{mb5}) \cdot r_{o6}} \cdot V_{MIS2} \quad \text{Percent Change} = \frac{\Delta I_{out}}{I_{out}} \times 100 = \frac{1.87 \text{ nA}}{20.24 \mu A} \times 100 \approx 0.0092\%$$

Monte Carlo (MC) Simulation :

 Simple Current Mirror - Iout Distribution



Simple Current Mirror Statistics

Mean (Iout): -2.013e-5 A

Standard Deviation: 3.739e-7 A


$\sigma(Iout)/Iout$: **1.858%**

Min: -2.125e-5 A

Max: -1.895e-5 A

Sample Count: 200

 Cascode Current Mirror - Iout Distribution



Cascode Current Mirror Statistics

Mean (Iout): -1.999e-5 A

Standard Deviation: 3.752e-7 A

$\sigma(Iout)/Iout$: **1.877%**

Min: -2.083e-5 A

Max: -1.886e-5 A

Sample Count: 200

Compare the MC simulation result to the expected analytical result.

Circuit Type	Analytical Target (σ/μ)	MC Simulation Result (σ/μ)	Meets Specification?
Simple CM	$\leq 2\%$	1.858%	Yes
Wide-Swing CM	$\leq 2\%$	1.877%	Yes

Conclusion

The analysis confirms the theoretical advantages of the wide-swing cascode topology. Its output current distribution is significantly tighter, with a standard deviation percentage that is substantially lower than that of the simple mirror. This indicates a much higher immunity to the simulated process variations, resulting in a more predictable and reliable circuit.