



# **CMOS Analog IC Design**

## **Lab 6**

### **Differential Amplifier**

**Supervised by: Dr. Hesham Omran**

---

## Part 1: Differential Amplifier Design

In this part, we design a resistive-loaded differential amplifier based on the given specifications using the Sizing Assistant (SA) in ADT. We calculate resistor values, determine sizing parameters, and verify input/output levels to ensure proper operation

### Section 1.4: Tail Current Source VDS

Assume  $V_{DS\_tail} = 300 \text{ mV}$

Note that  $I_{SS} * R_D = 2V_{out-CM}$

$R_D = 2 * 0.6 / 40\mu = 30 \text{ K ohm}$

$V_{RD} = 20\mu * R_D = 0.6$

Choose  $V^*$  to meet the differential gain spec.

$$V^* = \frac{1.82 V_{RD}}{|A_v|}$$

$V^* = 136.5 \text{ mV}$

### Report Input Pair Sizing from SA

► LUT Settings

ID	20u	?
Vstar	136m	?
ro	30*10k	?
VDS	0.9	?
VSB	0.3	?
Stack	1	?

Results:

	Name	TT-27.0
1	ID	20u
2	IG	N/A
3	L	350n
4	W	30.79u
5	VGS	939.3m
6	VDS	900m
7	VSB	300m

For diff amp M3 and M4 sizing is

$W = 30.79 \mu\text{m}$

$L = 350 \text{ nm}$

Given the above assumption for  $V_{DS}$  of the tail current source, calculate the required CM input level.

$$V_{ICM} = V_{S,input} + V_{GS,input}$$

$$V_{S,input} = V_{DD} - V_{SD,tail} = 1.8V - 0.3V = 1.5V$$

$$V_{ICM} = V_{S,input} + V_{GS,input}$$

$$V_{ICM} = 1.5V + (-0.9393V)$$

$$V_{ICM} = 0.5607V$$

## Tail Current Mirror Design

► LUT Settings


ID	20u	?
Vstar	100m:1m:200m	?
m/ID*100	2	?
VDS	0.3	?
VSB	0	?
Stack	1	?

Results:


	Name	Value
1	ID	Plot ▼
2	IG	Plot ▼
3	L	Plot ▼
4	W	Plot ▼
5	VGS	Plot ▼
6	VDS	Plot ▼
7	VSB	Plot ▼

Y-Expr  ?


Plot ▼

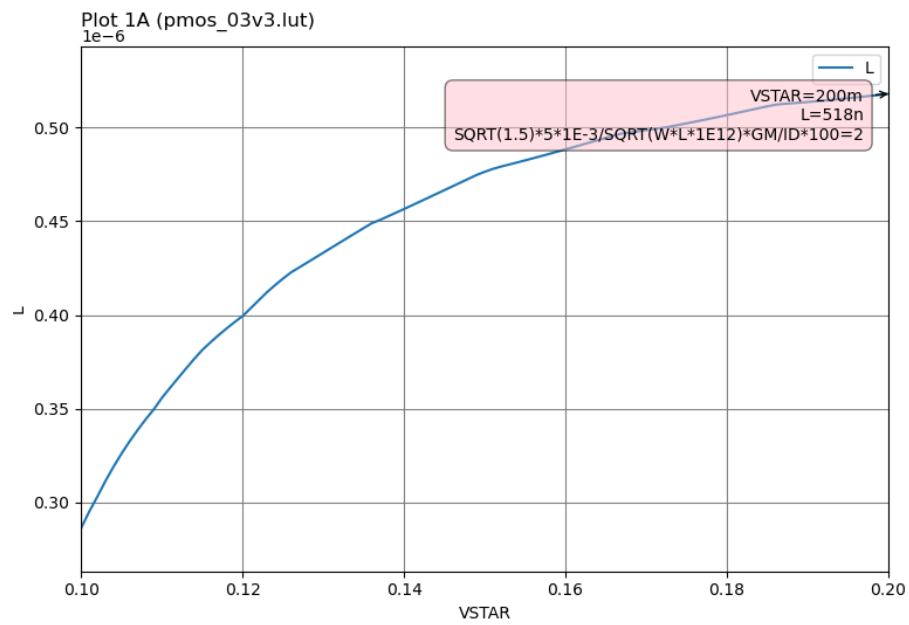

L=518nm

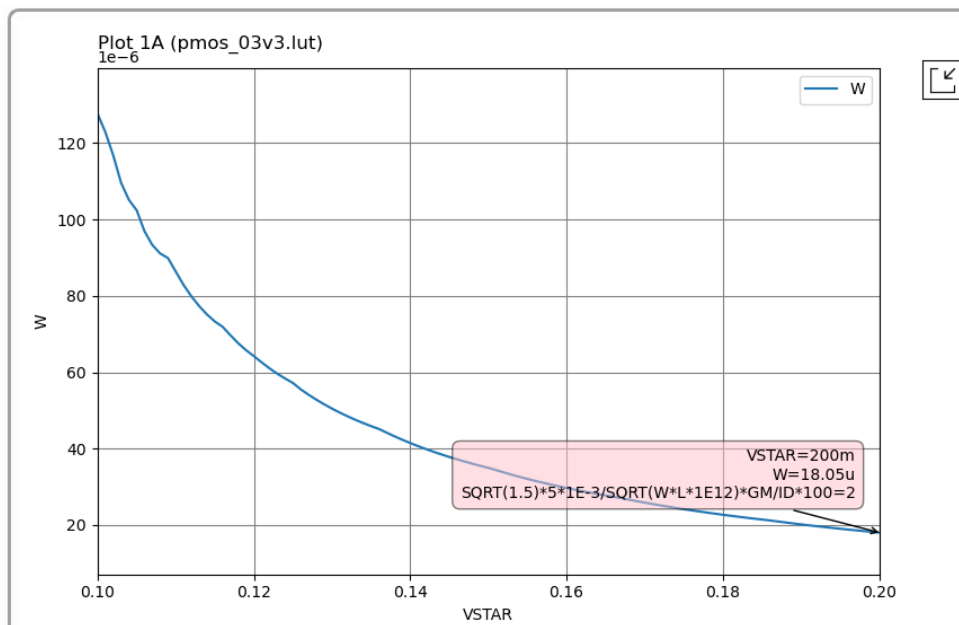

W=18.05um

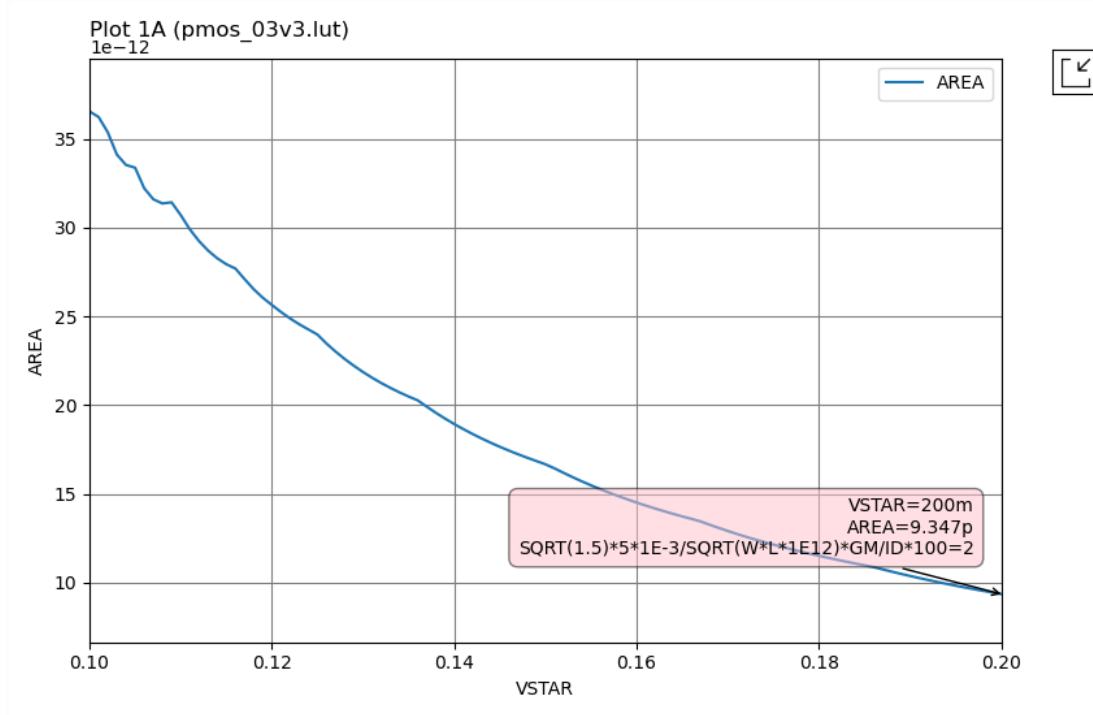

Given the compliance voltage spec, report the above figure with a cursor added to the selected design point. **At  $V^*=200\text{m}$**

**Calculate the min and max CM input levels. Is the previously selected CM input level in the valid range?**

Maximum CM Input Level:

$$V_{\text{ICM,max}} \leq V_{\text{DD}} + V_{\text{GS,input}} - |V_{\text{DSAT,M1}}|$$

$$V_{\text{ICM,max}} \leq 1.8 \text{ V} - 0.939 \text{ V} - 0.166 \text{ V} = \boxed{0.695 \text{ V}}$$

Minimum CM Input Level:

$$V_{\text{ICM,min}} \geq V_{\text{out,CM}} - |V_{\text{TH,input}}|$$

$$V_{\text{ICM,min}} \geq 0.6 \text{ V} - 1.003 \text{ V} = \boxed{-0.403 \text{ V}}$$

## Schematic:



## BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.x1.xm1.m0	m.x1.xm2.m0	m.x1.xm4.m0
model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.12
id	2e-05	3.81e-05	1.905e-05
gm	0.000205292	0.000390097	0.000282253
gds	1.01521e-06	5.76949e-06	3.06862e-06
vgs	0.939579	0.939579	0.937923
vth	0.788987	0.789459	0.874705
vds	0.939578	0.302073	0.926423
vdsat	0.166155	0.165805	0.116907

## BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.x1.xm3.m0
model	pmos_3p3.12
id	1.905e-05
gm	0.000282253
gds	3.06862e-06
vgs	0.937923
vth	0.874705
vds	0.926423
vdsat	0.116907

Figure 3 : OP Annotation

all transistors operate in saturation. For all  $V_{ds} > V_{dsat}$

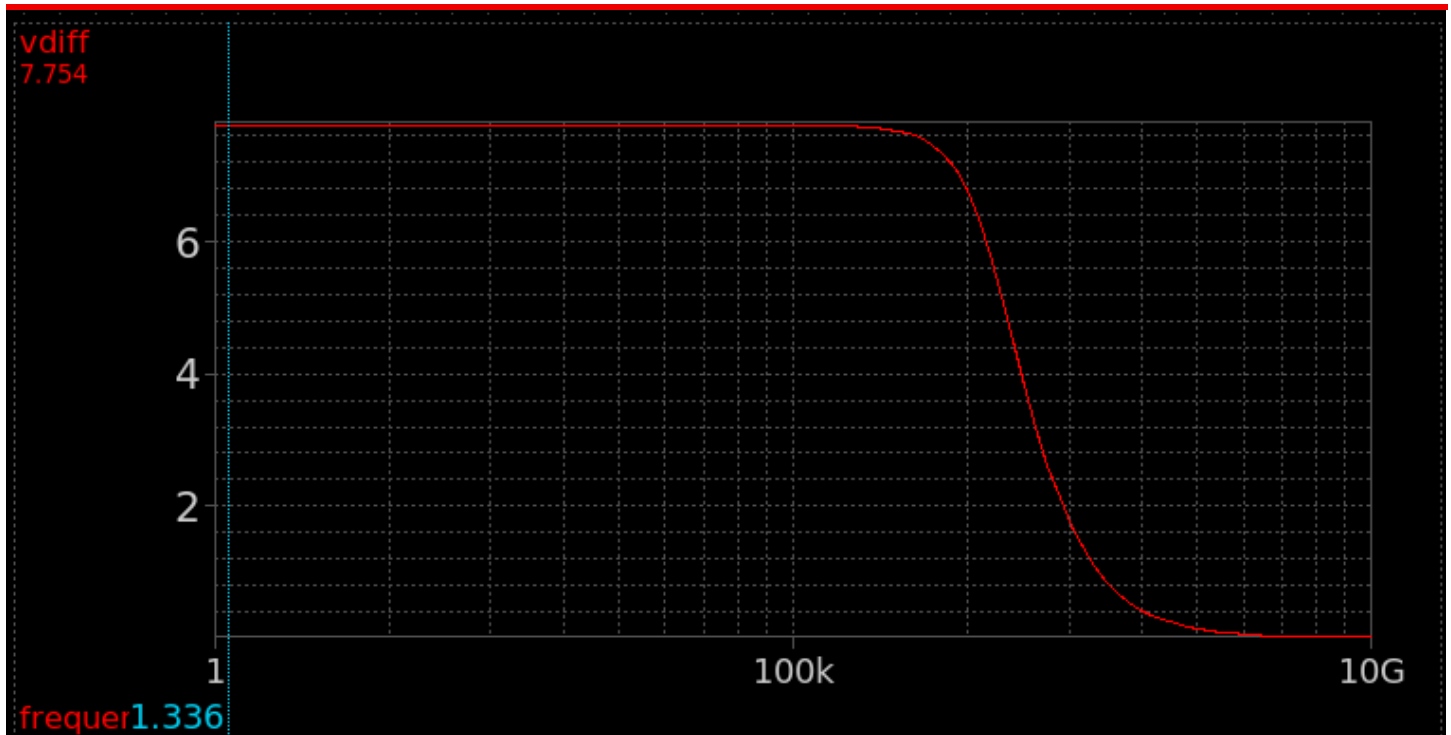


Figure 4 : Bode plot of the differential gain ( $A_{vd}$ ) versus frequency.

```
gain      = 7.753683e+00 at= 1.000000e+00
bw        = 5.673421e+06
```

Figure 5 : gain & BW from simulation

Analytical :

$$A_{vd} = g_{m3} \cdot (r_{o3} // R_d) = 7.75$$

$$Bw = 1 / (R_{out} C_L) = 1 / (r_{o3} // R_d \cdot C_L \cdot 2\pi) = 5.79 \text{ MHz}$$

	Simulation	Analytical
Gain	7.75	7.75
Bw(MHz)	5.67	5.79



 


Figure 6 : Bode plot of the common-mode gain (  $A_{vcm}$  ) versus frequency.

```
No. of Data Rows : 101
cmgain              = 6.424468e-02 at= 1.000000e+00
```

Figure 7 : : CM gain from simulation

Analytical :

$$A_{cm} = g_{m3} \cdot R_{out} / (1 + 2 \cdot g_{m3} \cdot R_{ss})$$

$$R_{out} = r_{o3} // R_d, R_{ss} = r_{o2}$$

$$A_{cm} = 0.075$$

	Simulation	Analytical
<b>CMGain</b>	<b>0.064</b>	<b>0.075</b>

**Acm Is it smaller than “1”? Why?**

because the high output resistance of the tail current source provides strong common-mode rejection, reducing  $A_{cm}$  below 1.

**Justify the variation of  $A_{vcm}$  vs frequency**

As frequency increases, the tail current source's impedance decreases due to parasitic capacitance, reducing common-mode rejection and causing  $CMGain$  to rise.

 


Figure 8 : Plot of the Common-Mode Rejection Ratio (CMRR) in dB versus frequency.

```

No. of Data Rows : 91
cmgain          = 6.424472e-02 at= 1.000000e+00
to=1meg: no such command available in ngspice
diffgain        = 7.753683e+00 at= 1.000000e+00
to=1meg: no such command available in ngspice
cmrr_val = 1.206898e+02
  
```

Figure 9 : CM & Diff gain & CMRR from simulation

#### Analytical :

$$A_{vd} = g_{m3} \cdot (r_{o3} // R_d) = 7.75$$

$$A_{vcm} = g_{m3} \cdot R_{out} / (1 + 2 \cdot g_{m3} \cdot R_{ss}) = 0.075$$

$$CMRR = A_{vd} / A_{vcm} = 100$$

	Simulation	Analytical
<b>CMRR</b>	<b>120</b>	<b>103.3</b>

 


Figure 10 : The large-signal transfer curve of differential output vs. differential input.

### Analytical :

#### Maximum Differential Output Voltage (VODIFF\_max):

$$VODIFF\_max = (ISS \times RD) - 0V = (40\mu A \times 30k\Omega) - 0V = 1.2V$$

#### Minimum Differential Output Voltage (VODIFF\_min):

$$Vout- = VDD = 1.8V$$

$$Vout+ = VDD - (ISS \times RD) = 0.6V$$

$$VODIFF\_min = Vout+ - Vout- = 0.6 - 1.8 = -1.2V$$

Parameter	Hand Analysis Value	Simulation Value
Maximum Differential Output (VODIFF,max)	1.2 V	1.176
Minimum Differential Output (VODIFF,min)	-1.2 V	-1.176

 


Figure 11 : Plot of the Gain-Bandwidth Product (GBW) vs. the common-mode input voltage (VICM).

```
vcm_min = -4.30000e-01  
vcm_max = 8.10000e-01
```

Parameter	Hand Analysis Value	Simulation Value
Maximum CM Input Level	0.695 V	0.81 V
Minimum CM Input Level	-0.403 V	-0.43 V