



CMOS Analog IC Design

Lab 11 (Mini Project 02)

Fully-Differential Folded Cascode OTA

Supervised by: Dr. Hesham Omran

PART 1: gm/ID Design Charts

Using ADT Sizing Assistant, plot the following design charts vs gm/ID for both PMOS and NMOS. Set VDS to a reasonable value and L = min, 1u:1u:5u.

- 1) VA
- 2) W/ID
- 3) fT
- 4) VGS

 


Figure 1 : VA vs gm/id for Nmos

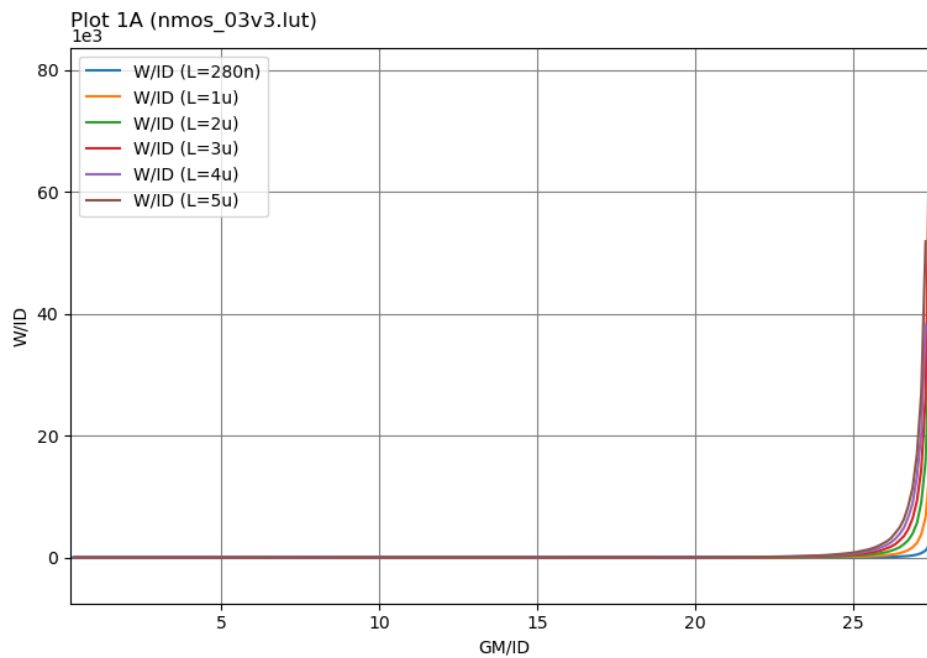
 
 


Figure 2 : W/ID vs gm/id for Nmos

Figure 3 : f_T vs g_m/i_d for NmosFigure 4 : V_{GS} vs g_m/i_d for Nmos

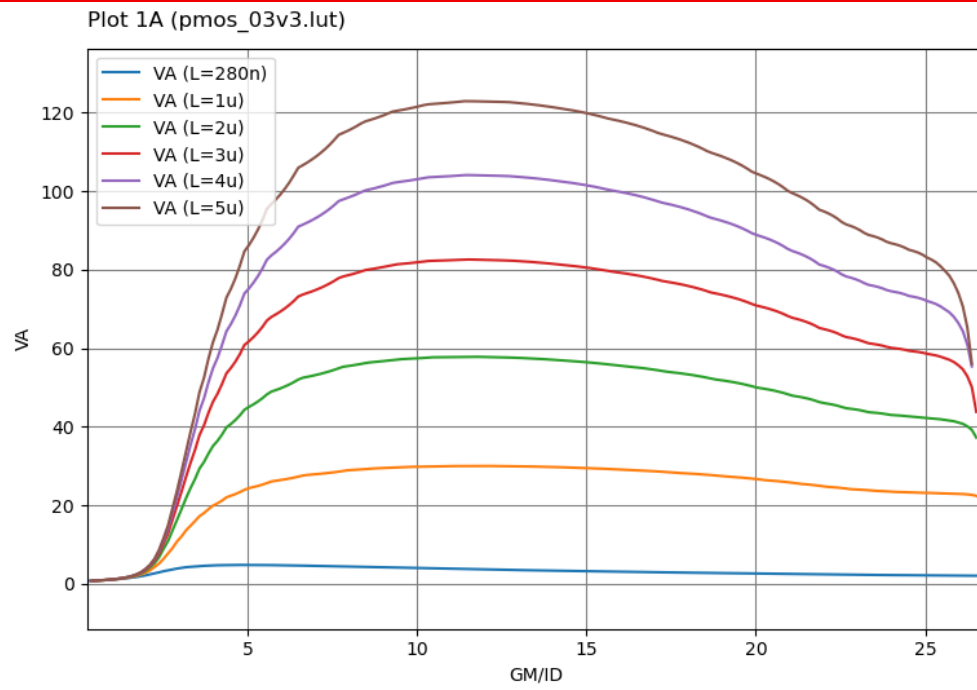


Figure 5 : VA vs gm/id for Pmos

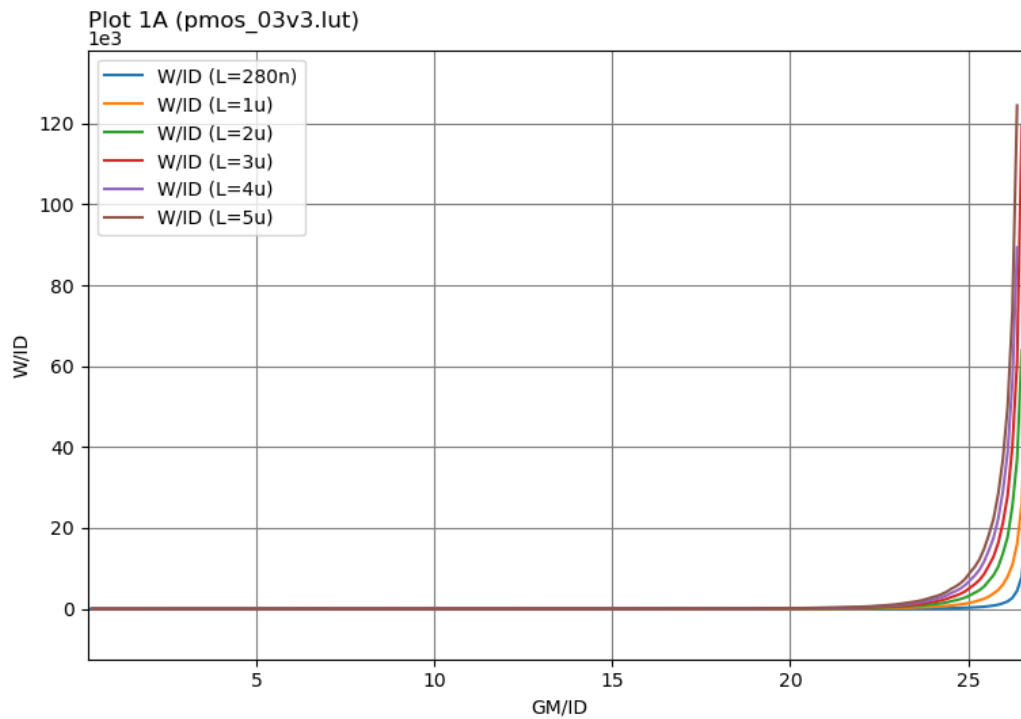


Figure 6 : W/ID vs gm/id for Pmos

 


Figure 7 : FT vs gm/id for Pmos

 


Figure 8 : VGS vs gm/id for Pmos

PART 2: OTA Design

Design a fully-differential folded cascode OTA with capacitive feedback that meets the specifications below. The current consumed in the biasing branches (current mirrors) is not included in the specifications.

Technology	GF180MCU
Supply Voltage	2.5 V
Closed-Loop Gain (ACL)	2
Phase Margin (PM)	$\geq 70^\circ$
CM Input Range – Low	≤ 0 V
CM Input Range – High	≥ 1 V
Differential Output Swing	1.2V _{pk-to-pk}
Load Capacitance (CL)	500fF
DC Loop Gain	≥ 60 dB
Settling Time (1% error)	≤ 100 ns

Design Procedure

- **Settling Time Specification**

Assume a first-order system for simplicity:

$$V_{out} = V_{in} (1 - e^{-(t/\tau)})$$

For 99% settling at $t = 100$ ns:

$$0.99 = 1 (1 - e^{-(100 \text{ ns}/\tau)}) \rightarrow \tau = 21.7 \text{ ns}$$

- **Closed-Loop Bandwidth**

$$BW_{cl} = 1 / (2\pi\tau) = 7.33 \text{ MHz}$$

- **Feedback Topology**

Voltage–Current feedback (Shunt–Shunt) with inverting amplifier configuration.

Feedback factor:

$$\beta = C_f / (C_{in} + C_f) = 1/3$$

- **Loop Gain Requirement**

$$\text{Loop Gain} = 1000 = \beta \times A_{ol}$$

$$A_{ol} = 3000 \text{ (with margin: } A_{ol} = 4000)$$

- **Gain–Bandwidth Product (GBW)**

$$GBW = BW_{cl} \times A_{cl} = 14.66 \text{ MHz}$$

$$\text{With margin: } GBW = 16 \text{ MHz}$$

- **Transconductance Requirement**

$$GBW = g_{m,in} / (2\pi \times C_{out})$$

$$C_{out} = C_L + C_f = 1.5 \text{ pF}$$

$$g_m = 150 \mu S$$

- **Bias Current Estimation**

Assuming $g_m/I_D = 15$:

$$I_D = 10 \mu A$$

- **GBW open**

$$GBW = g_{min}/2\pi \times C_L \rightarrow GBW = 48 \text{ MHz}$$

$$B_{wop} = GBW/A_{ol} > 15 \text{ KHz}$$

1)input pair Pmos

$$g_{m,input} \geq 150 \mu S$$

Assume $I_D = 10 \mu A$, $g_m/I_D = 17$, $L = 300 \text{ nm}$, $V_{ds} = 0.6$, $V_{SB} = 0$

LUT Settings

ID

10u

?

gm/ID

17

?

L

300n

?

VDS

0.6

?

VSB

0

?

Stack

1

?

Results:

	Name	TT-27.0
1	ID	10u
2	IG	N/A
3	L	300n
4	W	24.04u
5	VGS	773.3m
6	VDS	600m
7	VSB	0

Name		TT-27.0
8	gm/ID	16.91
9	Vstar	118.2m
10	fT	916.2MEG
11	gm/gds	60.39
12	VA	3.57
13	ID/W	416m
14	gm/W	7.036

Name		TT-27.0
16	gm	169.1u
17	gmb	59.4u
18	gds	2.801u
19	ro	357k
20	Ron	60k
21	VTH	745.6m
22	VDSAT	94.67m

2) Tail current mirror Pmos

The tail transistor will pass through it double the current of the input pair

$I_d = 20\mu$, $L = 1\mu\text{m}$, $g_m/I_d = 10$, $V_{DS} = 0.6$, $V_{SB} = 0$

ID	20u
gm/ID	10
L	1u
VDS	0.6
VSB	0
Stack	1

Results:

	Name	TT-27.0
8	gm/ID	9.896
9	Vstar	202.1m
10	fT	233MEG
11	gm/gds	295
12	VA	29.81
13	ID/W	510.9m
14	gm/W	5.056

Results:

	Name	TT-27.0
1	ID	20u
2	IG	N/A
3	L	1u
4	W	39.15u
5	VGS	943.4m
6	VDS	600m
7	VSB	0

	Name	TT-27.0
16	gm	197.9u
17	gmb	93.62u
18	gds	671n
19	ro	1.49MEG
20	Ron	30k
21	VTH	783.2m
22	VDSAT	156.4m

3) Tail current mirror Nmos

The tail transistor will pass through it double the current of the input pair

$I_d = 20\mu$, $L = 1\mu\text{m}$, $g_m/I_d = 10$, $V_{DS} = 0.6$, $V_{SB} = 0$

ID	20u	Results:	
gm/ID	10		
L	1u		
VDS	0.6		
VSB	0		
Stack	1		
Results:			
Name	TT-27.0	Name	TT-27.0
1 ID	20u	8 gm/ID	9.875
2 IG	N/A	9 Vstar	202.5m
3 L	1u	10 fT	1.153G
4 W	9.13u	11 gm/gds	249.4
5 VGS	836.3m	12 VA	25.26
6 VDS	600m	13 ID/W	2.191
7 VSB	0	14 gm/W	21.63
		16 gm	197.5u
		17 gmb	75.44u
		18 gds	791.8n
		19 ro	1.263MEG
		20 Ron	30k
		21 VTH	687m
		22 VDSAT	172.8m

5) cascode transistors Nmos

Assume $I_d = 10\mu$, $L = 0.5\mu$, $g_m/I_d = 15$, $V_{DS} = 0.6$, $V_{SB} = 0.3$

ID	10u	Results:	
gm/ID	15		
L	0.5u		
VDS	0.6		
VSB	0.3		
Stack	1		
Results:			
Name	TT-27.0	Name	TT-27.0
1 ID	10u	8 gm/ID	15
2 IG	N/A	9 Vstar	133.4m
3 L	500n	10 fT	2.207G
4 W	7.59u	11 gm/gds	131.7
5 VGS	849.9m	12 VA	8.784
6 VDS	600m	13 ID/W	1.318
7 VSB	300m	14 gm/W	19.76
		16 gm	150u
		17 gmb	45.77u
		18 gds	1.138u
		19 ro	878.4k
		20 Ron	60k
		21 VTH	807.8m
		22 VDSAT	110.8m

Sizing of VCASCN and VCASCP

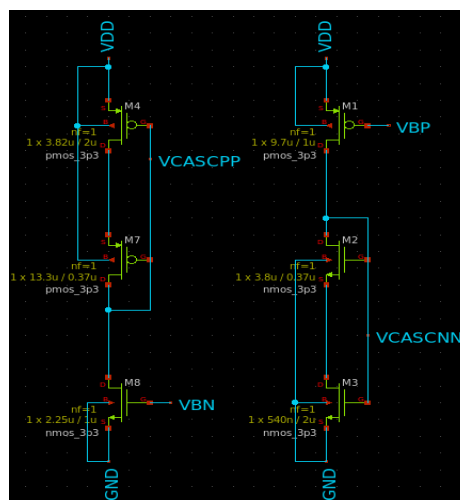


Figure 9 : Schematic of Replica Biasing

I will use a Replica Biasing

VCASCN (NMOS cascode bias)

PMOS current mirror (reference branch)

- Choose a fixed reference current:

$$I_{D,ref}=5\ \mu A$$

NMOS cascode device (replica)

- In a folded cascode, each NMOS cascode device carries **half of the branch current**:

$$I_{D,cascode}=\frac{I_{branch}}{2}$$

- To match this in the replica, size the cascode transistor as:

$$W_{cascode} = \frac{W_{main}}{2}, L_{cascode}=L$$

NMOS tail device (in replica)

we want $V_{GS} = 1.2$

assume $L = 2\mu$

Results:

Name		TT-27.0
1	ID	5.003u
2	IG	N/A
3	L	2u
4	W	540n

VCASCP (PMOS cascode bias)

NMOS current mirror (reference branch)

- Choose a fixed reference current:

$$I_{D,ref} = 5 \mu A$$

PMOS cascode device (replica)

- In a folded cascode, each PMOS cascode device carries **half of the branch current**:

$$I_{D,cascode} = \frac{I_{branch}}{2}$$

- To match this in the replica, size the cascode transistor as:

$$W_{cascode} = \frac{W_{main}}{2}, L_{cascode} = L$$

PMOS tail device (in replica)

we want $V_{GS} = 1.2$

assume $L = 2\mu$

Results:

Name		TT-27.0
1	ID	4.996u
2	IG	N/A
3	L	2u
4	W	3.82u
5	VGS	1.2

Transistor Sizing and Operating Point Summary:

Transistor Role	W (μm)	L (nm)	gm (μS)	ID (μA)	gm/ID	Vdsat (mV)	V* (mV)	VGS
Input Pair (PMOS)	24.04	300	169.1	10	17	94.67	118.2	0.773
Tail Mirror (PMOS)	39.15	1000	197.9	20	10	156.4	202.1	0.943
Tail Mirror (NMOS)	9.13	1000	197.5	20	10	172.8	202.5	0.836
Cascode (PMOS)	26.63	370	149.4	10	15	107.5	133.8	0.848
Cascode (NMOS)	7.59	370	150	10	15	110.8	133.4	0.849

From the assumed V^* , select suitable biasing for the cascode transistors (V_{CASCP} and V_{CASCN}).

$$V_{CASCN} \approx V_{GNS} + V^* = 0.85 + 0.14 = 0.99V = 1.2V \text{ with margin}$$

$$V_{CASCP} \approx V_{DD} - |V_{GSP}| - V^* = 2.5 - 0.85 - 0.2 = 1.45 = 1.2V \text{ with margin}$$

$$V_{incm,high} = V_{DD} - V_{GS,in} - V^* = 1.5249$$

$$V_{incm,low} = V_{thp} + V^*,_{CM_nmos} = 0.2025 V - 0.7456 V = -0.5431 V$$

$$V_{incm,middle} = 0.5V$$

$$V_{out,high} = V_{DD} - V^*,_{casc} - V_{GS} = 1.4232$$

$$V_{out,min} = V^*,_{casc} + V^*,_{CM} = 0.3359$$

$$V_{out,middle} = 0.88V$$

Note: I reduced the channel length of the cascode PMOS and NMOS devices from 500 nm to 370 nm in order to meet the specifications.

PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

Schematic of the OTA and bias circuit with DC node voltages and transistors OP parameters (id, vgs, vds, vdsat, vth, gm, gds, region) clearly annotated.

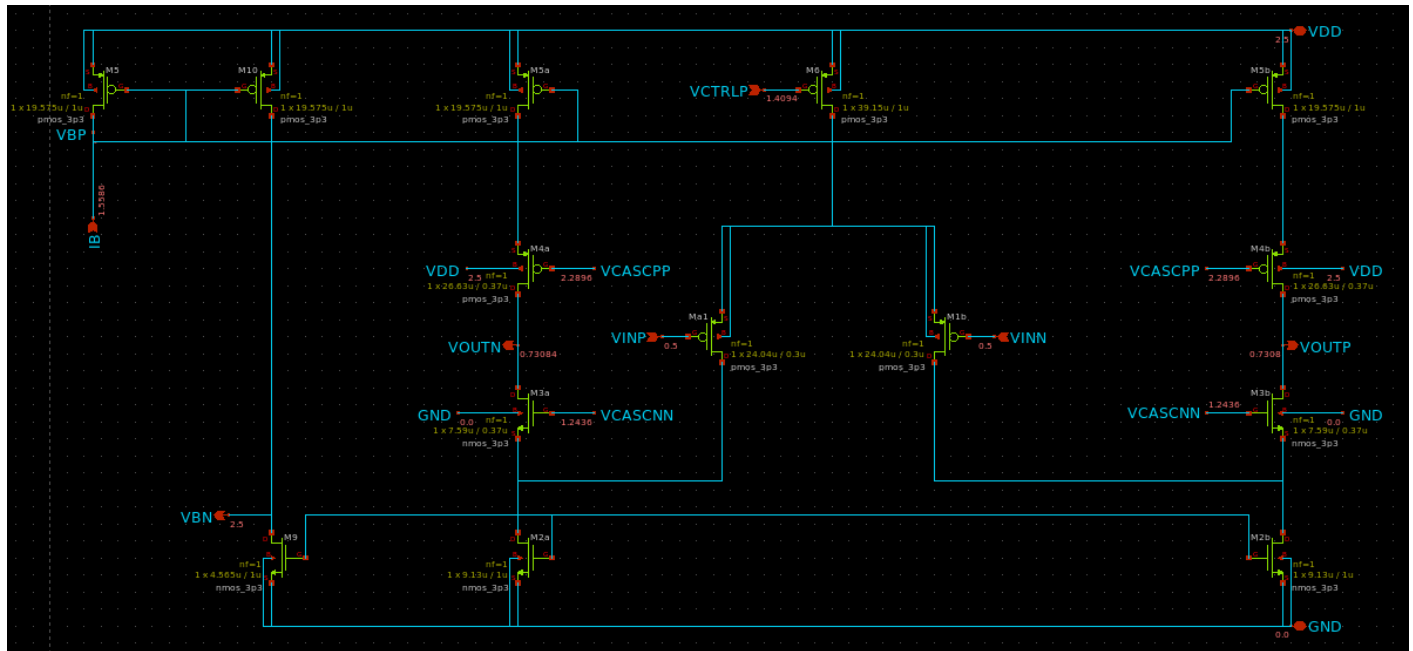


Figure 10 : Schematic of Fully-Differential Folded Cascode OTA

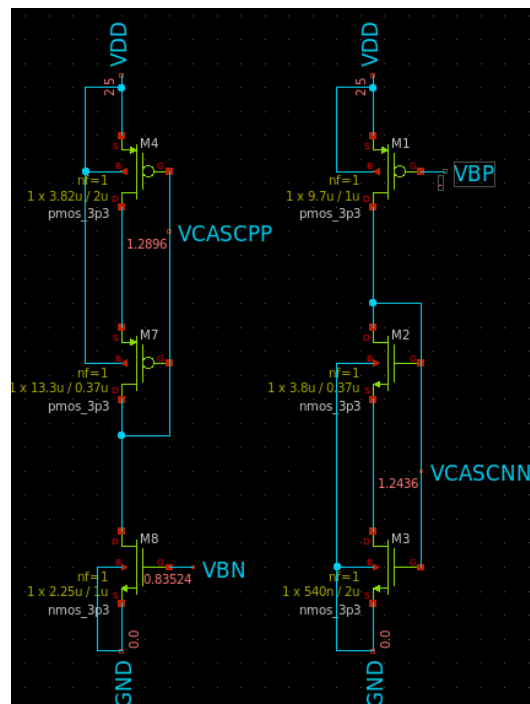


Figure 11 : Replica biasing



DC Operating point

BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.xm4_x1.m0	m.xm3_x1.m0	m.xm1_x1.m0	device	m.xm8_x1.m0	m.xm9_x1.m0	m.xm2b_x1.m0
model	pmos_3p3.10	nmos_3p3.6	pmos_3p3.9	model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9
id	4.90318e-06	4.99219e-06	4.99219e-06	id	4.90317e-06	1.01343e-05	2.02567e-05
gm	1.85813e-05	1.41853e-05	5.04236e-05	gm	4.8363e-05	0.000100841	0.000202541
gds	4.38492e-06	2.67182e-06	9.28769e-08	gds	1.43104e-07	3.30756e-07	1.03056e-06
vgs	1.21039	1.24357	0.941441	vgs	0.835242	0.835242	0.835242
vth	0.774877	0.654469	0.783923	vth	0.685215	0.687329	0.68835
vds	0.294425	0.427286	1.25641	vds	1.28961	0.835239	0.424534
vdsat	0.333805	0.473962	0.154389	vdsat	0.171291	0.172088	0.172481
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.xm2_x1.m0	m.xm3a_x1.m0	m.xm3b_x1.m0	device	m.xm2a_x1.m0	m.xm5_x1.m0	m.xm10_x1.m0
model	nmos_3p3.8	nmos_3p3.8	nmos_3p3.8	model	nmos_3p3.9	pmos_3p3.13	pmos_3p3.13
id	4.99219e-06	9.76045e-06	9.76045e-06	id	2.02567e-05	1e-05	1.01343e-05
gm	8.00452e-05	0.000156219	0.000156219	gm	0.000202541	0.000101062	0.000102318
gds	1.20001e-06	2.69973e-06	2.69961e-06	gds	1.03056e-06	2.29564e-07	1.55258e-07
vgs	0.816274	0.819044	0.819044	vgs	0.835242	0.941441	0.941441
vth	0.796201	0.799369	0.799368	vth	0.68835	0.783939	0.783937
vds	0.816272	0.451129	0.451186	vds	0.424533	0.94144	1.66475
vdsat	0.0978721	0.0980206	0.0980203	vdsat	0.172481	0.154376	0.154377
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.xm5b_x1.m0	m.xm5a_x1.m0	m.xm6_x1.m0	device	m.x1.xma1.m0	m.x1.xm1b.m0	
model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.13	model	pmos_3p3.12	pmos_3p3.12	
id	9.7605e-06	9.7605e-06	2.09926e-05	id	1.04963e-05	1.04963e-05	
gm	9.83378e-05	9.83378e-05	0.000208322	gm	0.000177642	0.000177642	
gds	9.0601e-07	9.06008e-07	3.96322e-07	gds	2.69568e-06	2.69568e-06	
vgs	0.941441	0.941441	0.945741	vgs	0.775221	0.775221	
vth	0.783941	0.783941	0.783938	vth	0.747643	0.747643	
vds	0.297248	0.297248	1.22478	vds	0.850682	0.850681	
vdsat	0.154374	0.154374	0.157318				
BSIM4v5: Berkeley Short Channel IGFET Model-4							
device	m.xm7_x1.m0	m.xm4b_x1.m0	m.xm4a_x1.m0				
model	pmos_3p3.12	pmos_3p3.12	pmos_3p3.12				
id	4.90318e-06	9.76049e-06	9.76049e-06				
gm	8.15537e-05	0.000163126	0.000163126				
gds	7.25457e-07	1.31426e-06	1.31425e-06				
vgs	0.915958	0.913137	0.913137				
vth	0.880994	0.879986	0.879986				
vds	0.915958	1.32702	1.32708				

Set VICM at the middle of the CMIR

Vincm,middle = 0.5V

Select VREF to maximize the symmetrical output swing.

VREF = VDD/2 = 1.25 V

What is the CM level at the OTA output?

Vocm = 1.2457 V

What are the differential input and output voltages of the error amplifier? What is the relation between them?

$\Delta V_{idiff} = V_{ref} - V_{ocm} = 1.25 \text{ mV} - 1.2457 \text{ mV} = 4.3 \text{ mV}$

$\Delta V_{odiff} = V_{BP} - V_{CTRLP} = 1.558559 - 1.554193 = 4.3 \text{ mV}$

$\frac{\Delta V_{odiff}}{\Delta V_{idiff}} = \frac{4.3 \text{ mV}}{4.3 \text{ mV}} = 1 \text{V (Buffer)}$

2) Diff small signal ccs:

- Use AC analysis (1Hz:10Gz, logarithmic, 10 points/decade).
- Plot diff gain (magnitude in dB and phase) vs frequency.

 


Figure 14 : diff gain (magnitude in dB and phase) vs frequency

```
gain          = 3.519799e+03 at= 1.000000e+00
bw            = 1.494257e+04
ugf           = 5.281160e+07
gbw = 5.259484e+07
```

Figure 15 : Open Loop Gain and BW form simulation (Behavioral CMFB)

From simulation $PM = 180 + Ph(UGF) = 180 + -95.784 = 84.2^\circ$

- Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

DC gain = GM Rout

$$R_{out} = R_{out,up} // R_{out,down}$$

$$R_{out,up} \approx r_{o4}(1 + g_{m4} \cdot r_{o5}) = 137.6 \text{ M}\Omega$$

$$R_{out,down} \approx r_{o3}(1 + g_{m3} \cdot (r_{o2} // r_{o1})) = 15.882 \text{ M}\Omega$$

$$GM = g_{m,input} = 177.642 \mu S$$

$$DC \text{ gain} = 68.06 \text{ dB}$$

$$Bw = \frac{1}{2\pi \cdot R_{out} \cdot C_{out}} \rightarrow C_{out} = 0.5 + 0.1(\text{parasitic}) = 0.6 \rightarrow Bw = 18.63 \text{ KHz}$$

$$GBW = DC \text{ gain} \cdot Bw = 51.4 \text{ MHz} = UGF$$

$$W_{nd2} = \frac{g_{m,M3a}}{2\pi(C_{ss,M3a} + C_{dd,M2a} + C_{dd,Ma1a})} \rightarrow CDD1 = 15.49 \text{ f}, CDD2 = 8.811 \text{ f}, CSS = 55.8 \text{ f} \rightarrow W_{p2} = 310.8 \text{ MHz}$$

$$PM = 90 - \tan^{-1} \left(\frac{W_{p2}}{W_u} \right) = 88.59^\circ$$

Parameter	Hand Analysis	Simulation Result
DC Gain	68.06 dB	70.9 dB
Bandwidth (BW)	18.63 kHz	14.9 kHz
GBW / UGF	51.4 MHz	52.8 MHz
PM	88.59°	84.2°

Sizing of M1 ,M2 ,M11

Assume $i_d = 5\mu$ gm/id =15 , L = 1u Vds = 0.6

Results:

	Name	TT-27.0
1	ID	5u
2	IG	N/A
3	L	1u
4	W	32.26u
5	VGS	846.5m
6	VDS	600m

Sizing of M3 ,M4 ,M7 ,M8 ,M10

Will be a ratio from Tail Current mirror Pmos

$I_d = 5\mu$ then the $W = \frac{W_{tail}}{2} = 9.7\mu$, $L = L_{tail} = 1\mu$

For input pair Nmos M5,M6

Assume $i_d = 5\mu$ gm/id =15 , L = 1u Vds = 0.6

Results:

	Name	TT-27.0
1	ID	5u
2	IG	N/A
3	L	1u
4	W	7.24u
5	VGS	742.4m
6	VDS	600m

Sizing of NMOS Error Amp Tail Source

Will be a ratio from Tail Current mirror Pmos

$I_d = 5\mu$ then the $W = \frac{W_{tail}}{2} = 4.565\mu$, $L = L_{tail} = 1\mu$

- The branch M10 and M11 is to add the Dc shift (offset) to Vref Like Vocm

Transistor Name(s)	Role in CMFB Circuit	W (μm)	L (μm)
M1, M2 ,M11	PMOS Source Followers	32.26	1
M3 ,M4 ,M7 ,M8 ,M10	PMOS Source Follower Bias	9.7	1
M5, M6	NMOS Error Amp Input Pair	4.565	1
M9	NMOS Error Amp Tail Source	4.565	1

1) Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters (id, vgs, vds, vdsat, vth, gm, gds, region) clearly annotated.

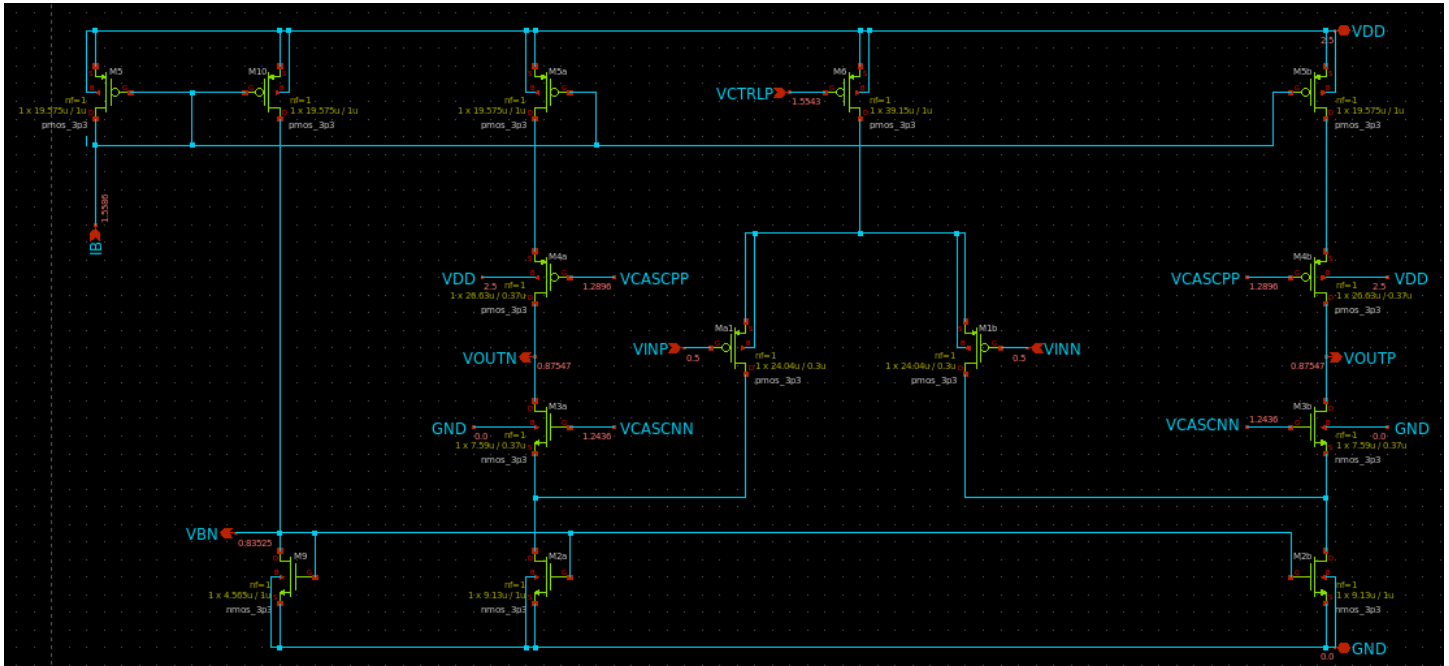


Figure 17 : : Schematic of Fully-Differential Folded Cascode OTA

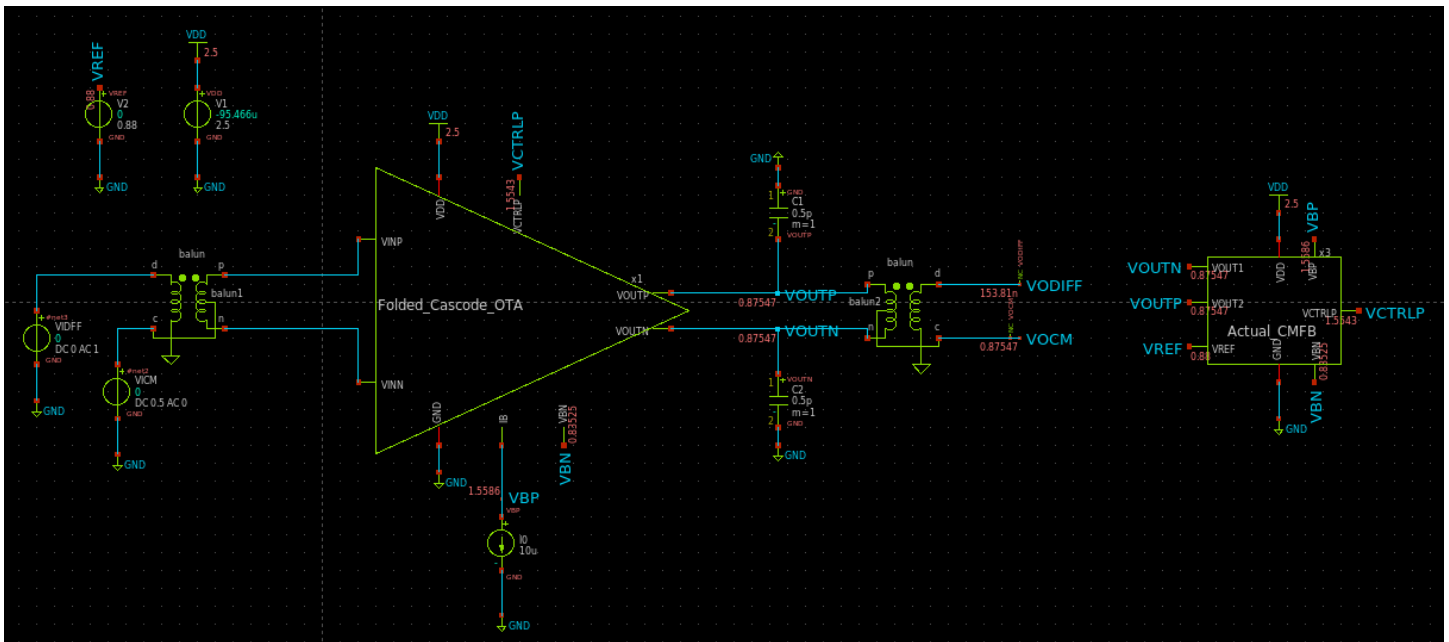


Figure 18 : open-loop testbench for simulating a folded-cascode OTA with Actual CMFB circuit

DC Operating point

BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm4.m0	m.x1.xm3.m0	m.x3.xm10_cmb.m0	device	m.x3.xm3_cmb.m0	m.x1.xm1.m0	m.x1.xm2.m0
model	pmos_3p3.10	nmos_3p3.6	pmos_3p3.9	model	pmos_3p3.9	pmos_3p3.9	nmos_3p3.8
id	4.90317e-06	4.99219e-06	4.93972e-06	id	4.94031e-06	4.9922e-06	4.9922e-06
gm	1.85813e-05	1.41853e-05	4.9917e-05	gm	4.9923e-05	5.04236e-05	8.00452e-05
gds	4.38491e-06	2.67182e-06	1.31672e-07	gds	1.31084e-07	9.2877e-08	1.20001e-06
vgs	1.21038	1.24357	0.941441	vgs	0.941441	0.941441	0.816274
vth	0.774877	0.654469	0.783924	vth	0.783924	0.783923	0.796201
vds	0.294425	0.427286	0.775989	vds	0.780508	1.25641	0.816272
vdsat	0.333805	0.473963	0.154388	vdsat	0.154388	0.154389	0.0978722
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x3.xm8_cmb.m0	m.x3.xm7_cmb.m0	m.x3.xm4_cmb.m0	device	m.x1.xm3a.m0	m.x1.xm3b.m0	m.x3.xm9_cmb.m0
model	pmos_3p3.9	pmos_3p3.9	pmos_3p3.9	model	nmos_3p3.8	nmos_3p3.8	nmos_3p3.9
id	5.22149e-06	4.88044e-06	4.94031e-06	id	9.76051e-06	9.76051e-06	1.01019e-05
gm	5.18245e-05	4.98125e-05	4.9923e-05	gm	0.000156219	0.000156219	0.000100597
gds	1.19302e-07	1.12395e-07	1.31084e-07	gds	2.70017e-06	2.70017e-06	3.49702e-07
vgs	0.945741	0.939045	0.941441	vgs	0.819048	0.819048	0.835242
vth	0.783928	0.783928	0.783924	vth	0.799369	0.799369	0.687329
vds	0.94574	0.939044	0.780508	vds	0.45093	0.45093	0.739779
vdsat	0.157326	0.152752	0.154388				
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x3.xm5_cmb.m0	m.x3.xm6_cmb.m0	m.x1.xm8.m0	device	m.x3.xm11_cmb.m0	m.x3.xm1_cmb.m0	m.x3.xm2_cmb.m0
model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9	model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.13
id	5.22149e-06	4.88044e-06	4.90317e-06	id	4.93971e-06	4.94031e-06	4.94031e-06
gm	7.76219e-05	7.39483e-05	4.8363e-05	gm	7.52933e-05	7.52933e-05	7.52933e-05
gds	2.06866e-07	1.96421e-07	1.43104e-07	gds	8.70546e-08	8.71843e-08	8.71843e-08
vgs	0.984224	0.979706	0.835242	vgs	0.844009	0.844022	0.844022
vth	0.928611	0.928611	0.685215	vth	0.783937	0.783937	0.783937
vds	0.814472	0.821168	1.28961	vds	1.72401	1.71949	1.71949
vdsat	0.115275	0.112445	0.171291	vdsat	0.0935863	0.0935934	0.0935934
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm5a.m0	m.x1.xm2b.m0	m.x1.xm2a.m0	device	m.x1.xm5.m0	m.x1.xm10.m0	m.x1.xm5b.m0
model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9	model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.13
id	1.01343e-05	2.02568e-05	2.02568e-05	id	1e-05	1.01343e-05	9.7605e-06
gm	0.000100841	0.000202541	0.000202541	gm	0.000101062	0.000102318	9.83378e-05
gds	3.30756e-07	1.03057e-06	1.03057e-06	gds	2.29564e-07	1.55258e-07	9.06001e-07
vgs	0.835242	0.835242	0.835242	vgs	0.941441	0.941441	0.941441
vth	0.687329	0.68835	0.68835	vth	0.783939	0.783937	0.783941
vds	0.835239	0.42453	0.42453	vds	0.94144	1.66475	0.297249
vdsat	0.172088	0.172481	0.172481	vdsat	0.154376	0.154377	0.154374
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm5a.m0	m.x1.xm6.m0	m.x1.xm7.m0	device	m.x1.xm1b.m0		
model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.12	model	pmos_3p3.12		
id	9.7605e-06	2.09925e-05	4.90317e-06	id	1.04963e-05		
gm	9.83378e-05	0.000208321	8.15537e-05	gm	0.000177642		
gds	9.06001e-07	3.9632e-07	7.25456e-07	gds	2.69567e-06		
vgs	0.941441	0.945741	0.915958	vgs	0.775221		
vth	0.783941	0.783938	0.880994	vth	0.747643		
vds	0.297249	1.22478	0.915957	vds	0.850685		
vdsat	0.154374	0.157317	0.0986095	vdsat	0.0942001		
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm4b.m0	m.x1.xm4a.m0	m.x1.xm1a.m0				
model	pmos_3p3.12	pmos_3p3.12	pmos_3p3.12				
id	9.76051e-06	9.76051e-06	1.04963e-05				
gm	0.000163126	0.000163126	0.000177642				
gds	1.3142e-06	1.3142e-06	2.69567e-06				
vgs	0.913135	0.913135	0.775221				
vth	0.879985	0.879985	0.747643				
vds	1.32728	1.32728	0.850685				
vdsat	0.0975983	0.0975983	0.0942001				

What is the CM level at the OTA output? Why?

vocm = 0.875 The OTA output CM level settles at ~0.875 V because the CMFB loop forces the outputs to track the reference voltage (Vref = 0.88 V).

What are the differential input and output voltages of the error amplifier? What is the relation between them?

$$\Delta V_{diff} = V_{ref} - V_{ocm} = 880.0 \text{ mV} - 875 \text{ mV} = 5 \text{ mV}$$

$$\Delta V_{odiff} = V_{BP} - V_{CTRLP} = 1.558559 - 1.554258 = 4.3 \text{ mV}$$

$$\frac{\Delta V_{odiff}}{\Delta V_{diff}} = \frac{4.3 \text{ mV}}{5 \text{ mV}} = 0.86V$$

They are not exactly equal because the relation between them is the gain error amplifier.

2) Diff small signal ccs:

- Use AC analysis (1Hz:10Gz, logarithmic, 10 points/decade).
- Plot diff gain (magnitude in dB and phase) vs frequency.

 


Figure 19 : diff gain (magnitude in dB and phase) vs frequency

```
gain      = 3.121452e+03 at= 1.000000e+00
bw        = 1.644323e+04
ugf       = 5.102532e+07
gbw = 5.132675e+07
```

Figure 20 : Open Loop Gain and BW form simulation (Actual CMFB)

From simulation $PM = 180 + Ph(UGF) = 180 + -95.287 = 84.7^\circ$

- Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

DC gain = GM Rout

$$R_{out} = R_{out,up} // R_{out,down}$$

$$R_{out,up} \approx r_{o4}(1 + g_{m4} \cdot r_{o5}) = 137.5 \text{ M}\Omega$$

$$R_{out,down} \approx r_{o3}(1 + g_{m3} \cdot (r_{o2} // r_{o1})) = 15.88 \text{ M}\Omega$$

$$GM = g_{m,input} = 177.642 \mu S$$

$$DC \text{ gain} = 68.06 \text{ dB}$$

$$Bw = \frac{1}{2\pi \cdot R_{out} \cdot C_{out}} \rightarrow C_{out} = 0.5 + 0.1 (\text{parasitic}) = 0.6 \rightarrow Bw = 18.63 \text{ KHz}$$

$$GBW = DC \text{ gain} \cdot Bw = 51.4 \text{ MHz} = UGF$$

$$W_{nd2} = \frac{g_{m,M3a}}{2\pi(C_{ss,M3a} + C_{dd,M2a} + C_{dd,Ma1a})} \rightarrow CDD1 = 15.49 \text{ f}, CDD2 = 8.811 \text{ f}, CSS = 55.8 \text{ f} \rightarrow W_{p2} = 310.8 \text{ MHz}$$

$$PM = 90 - \tan^{-1} \left(\frac{W_{p2}}{W_u} \right) = 88.59^\circ$$

Parameter	Hand Analysis	Simulation Result
DC Gain	68.06 dB	69.89 dB
Bandwidth (BW)	18.63 kHz	16.44 kHz
GBW / UGF	51.4 MHz	51.02 MHz
PM	88.59°	84.7°

PART 5: Closed Loop Simulation (AC and STB Analysis)

Create a new testbench with the OTA connected in closed-loop feedback configuration using capacitive feedback as shown below. Note that the CM DC level provided before the input balun is useless because it is blocked by the capacitor.

- 1) Schematic of the OTA and the CMFB circuit with DC OP point clearly annotated in closed-loop configuration.

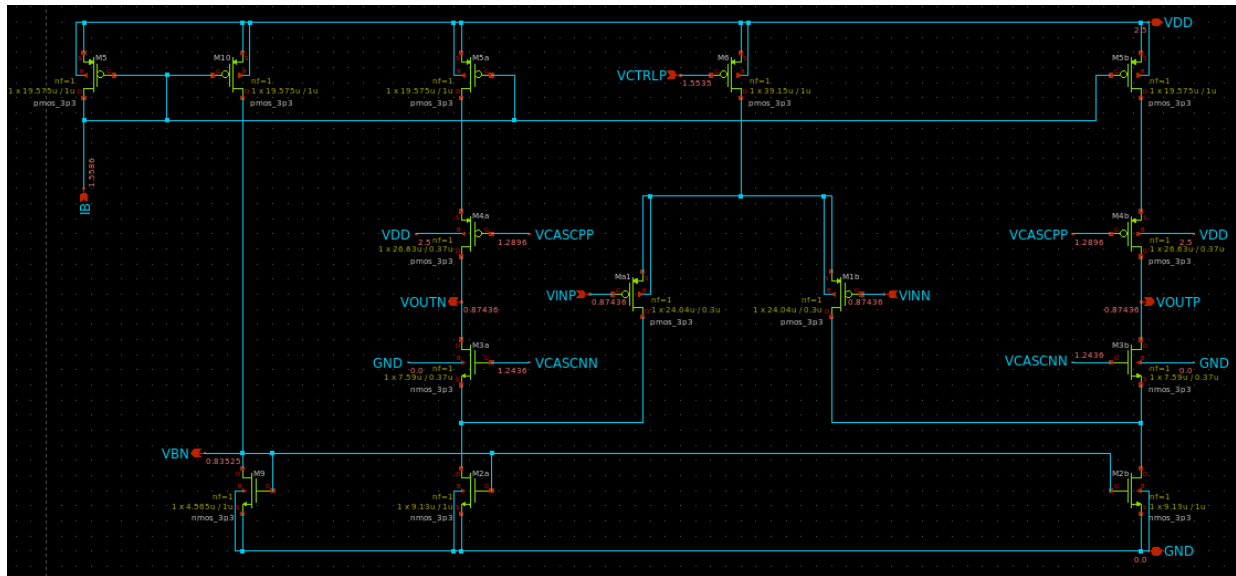


Figure 21 : Schematic of Fully-Differential Folded Cascode OTA


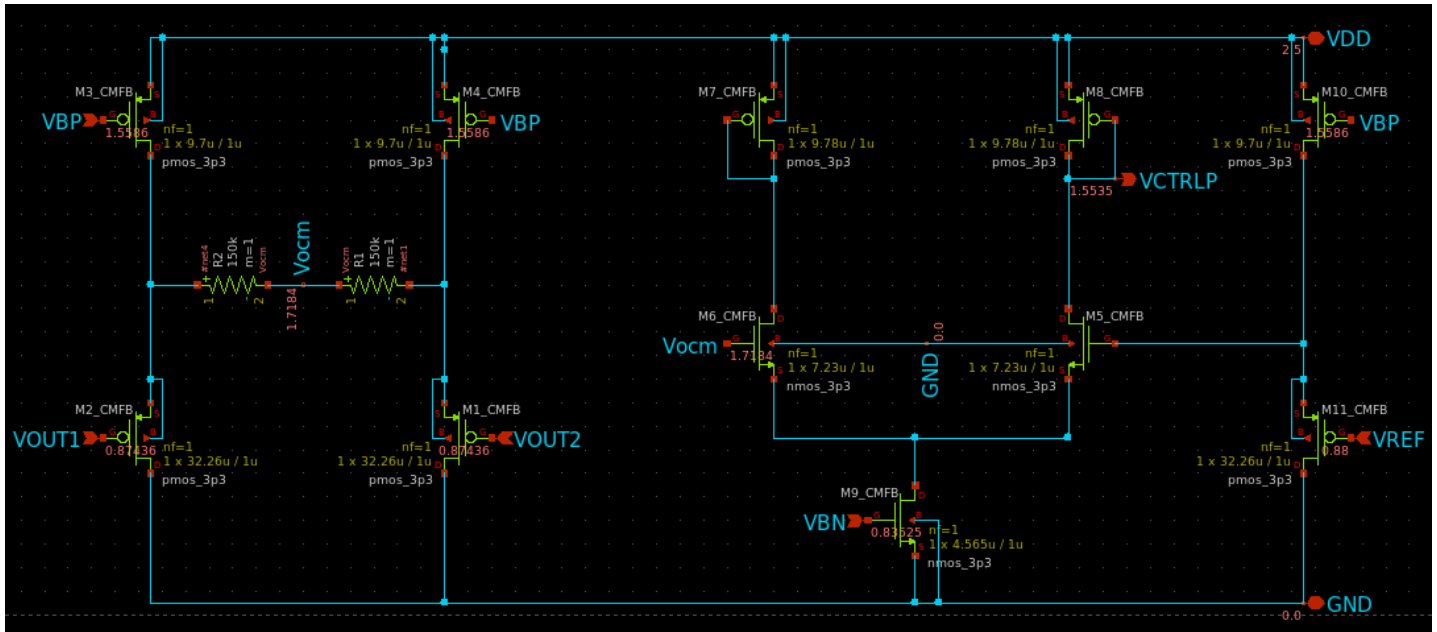


Figure 22 : Actual CMFB

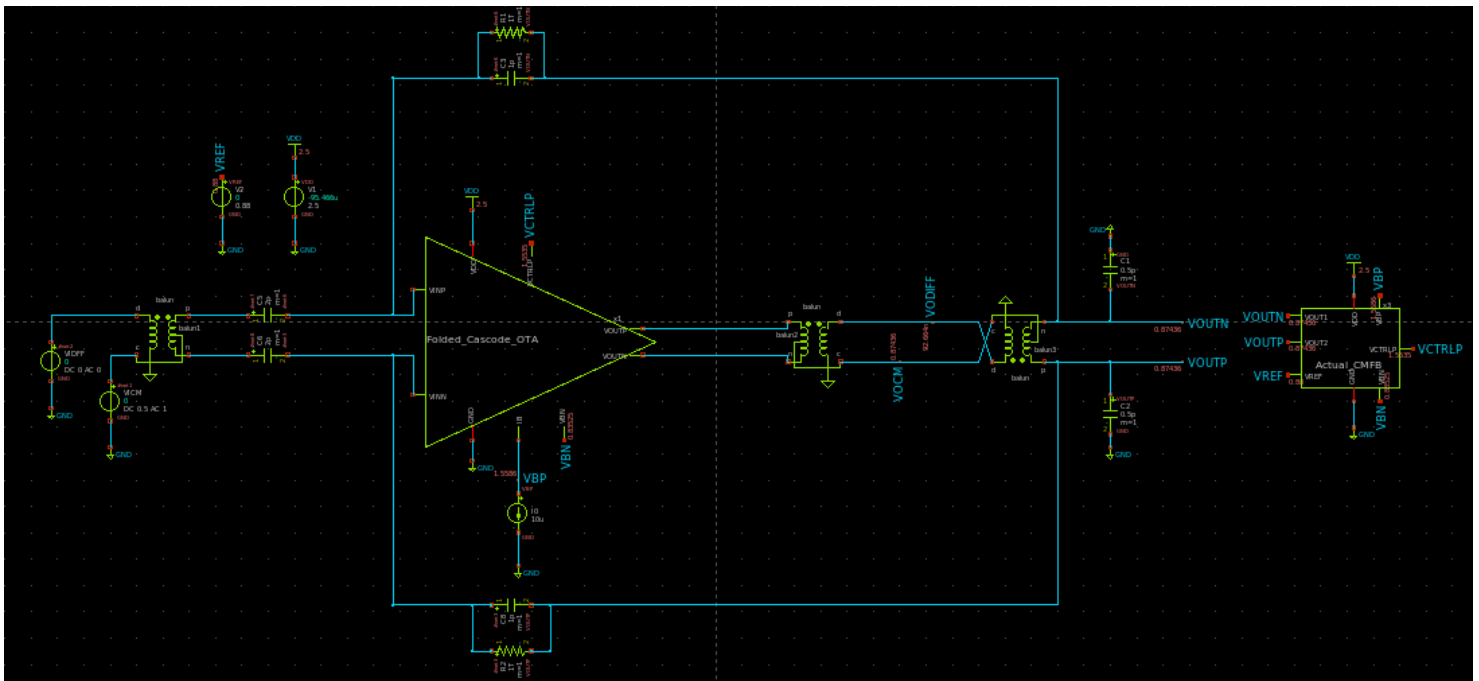

DC Operating point

BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm4.m0	m.x1.xm3.m0	m.x3.xm10_cmb.m0	device	m.x3.xm3_cmb.m0	m.x1.xm1.m0	m.x1.xm2.m0
model	pmos_3p3.10	nmos_3p3.6	pmos_3p3.9	model	pmos_3p3.9	pmos_3p3.9	nmos_3p3.8
id	4.90317e-06	4.99219e-06	4.93972e-06	id	4.94045e-06	4.9922e-06	4.9922e-06
gm	1.85813e-05	1.41853e-05	4.9917e-05	gm	4.99244e-05	5.04236e-05	8.00452e-05
gds	4.38491e-06	2.67182e-06	1.31672e-07	gds	1.30942e-07	9.2877e-08	1.20001e-06
vgs	1.21038	1.24357	0.941441	vgs	0.941441	0.941441	0.816274
vth	0.774877	0.654469	0.783924	vth	0.783924	0.783923	0.796201
vds	0.294425	0.427286	0.775989	vds	0.781611	1.25641	0.816272
vdsat	0.333805	0.473963	0.154388	vdsat	0.154388	0.154389	0.0978722
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x3.xm8_cmb.m0	m.x3.xm7_cmb.m0	m.x3.xm4_cmb.m0	device	m.x1.xm3a.m0	m.x1.xm3b.m0	m.x3.xm9_cmb.m0
model	pmos_3p3.9	pmos_3p3.9	pmos_3p3.9	model	nmos_3p3.8	nmos_3p3.8	nmos_3p3.9
id	5.26302e-06	4.83876e-06	4.94045e-06	id	9.7605e-06	9.76051e-06	1.01018e-05
gm	5.2064e-05	4.95608e-05	4.99244e-05	gm	0.000156216	0.000156217	0.000100595
gds	1.2014e-07	1.11548e-07	1.30942e-07	gds	2.70251e-06	2.70251e-06	3.49799e-07
vgs	0.946539	0.939208	0.941441	vgs	0.819063	0.819063	0.835242
vth	0.783928	0.783928	0.783924	vth	0.799374	0.799374	0.687329
vds	0.946538	0.938207	0.781611	vds	0.449838	0.449838	0.739363
vdsat	0.157873	0.152183	0.154388	vdsat	0.098027	0.0980271	0.172087
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x3.xm5_cmb.m0	m.x3.xm6_cmb.m0	m.x1.xm8.m0	device	m.x3.xm11_cmb.m0	m.x3.xm1_cmb.m0	m.x3.xm2_cmb.m0
model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9	model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.13
id	5.26302e-06	4.83876e-06	4.90317e-06	id	4.93971e-06	4.94045e-06	4.94045e-06
gm	7.80621e-05	7.34919e-05	4.8363e-05	gm	7.52933e-05	7.53008e-05	7.53008e-05
gds	2.08111e-07	1.9512e-07	1.43104e-07	gds	8.70546e-08	8.7216e-08	8.72161e-08
vgs	0.98464	0.979019	0.835242	vgs	0.844009	0.844025	0.844026
vth	0.928494	0.928494	0.685215	vth	0.783937	0.783937	0.783937
vds	0.814091	0.822421	1.28961	vds	1.72401	1.71839	1.71839
vdsat	0.115611	0.112089	0.171291	vdsat	0.0935863	0.0935951	0.0935951
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm9.m0	m.x1.xm2b.m0	m.x1.xm2a.m0	device	m.x1.xm5.m0	m.x1.xm10.m0	m.x1.xm5b.m0
model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9	model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.13
id	1.01343e-05	2.02567e-05	2.02567e-05	id	1e-05	1.01343e-05	9.76051e-06
gm	0.000100841	0.000202541	0.000202541	gm	0.000101062	0.000102318	9.83379e-05
gds	3.30756e-07	1.03061e-06	1.03061e-06	gds	2.29564e-07	1.55258e-07	9.05948e-07
vgs	0.835242	0.835242	0.835242	vgs	0.941441	0.941441	0.941441
vth	0.687329	0.68835	0.68835	vth	0.783939	0.783937	0.783941
vds	0.835239	0.424515	0.424515	vds	0.94144	1.66475	0.297256
vdsat	0.172088	0.172481	0.172481	vdsat	0.154376	0.154377	0.154374
BSIM4v5: Berkeley Short Channel IGFET Model-4				BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm5a.m0	m.x1.xm6.m0	m.x1.xm7.m0	device	m.x1.xm1b.m0		
model	pmos_3p3.13	pmos_3p3.13	pmos_3p3.12	model	pmos_3p3.12		
id	9.76051e-06	2.09925e-05	4.90317e-06	id	1.04962e-05		
gm	9.83379e-05	0.000207708	8.15537e-05	gm	0.000178321		
gds	9.05948e-07	5.17533e-07	7.25456e-07	gds	2.50993e-06		
vgs	0.941441	0.946539	0.915958	vgs	0.769844		
vth	0.783941	0.78394	0.880994	vth	0.744238		
vds	0.297256	0.855792	0.915957	vds	1.21969		
vdsat	0.154374	0.157864	0.0986095	vdsat	0.0931265		
BSIM4v5: Berkeley Short Channel IGFET Model-4							
device	m.x1.xm4b.m0	m.x1.xm4a.m0	m.x1.xm1a.m0				
model	pmos_3p3.12	pmos_3p3.12	pmos_3p3.12				
id	9.76051e-06	9.76051e-06	1.04962e-05				
gm	0.000163128	0.000163128	0.000178321				
gds	1.31395e-06	1.31395e-06	2.50993e-06				
vgs	0.913129	0.913129	0.769845				
vth	0.879982	0.879982	0.744238				
vds	1.32838	1.32838	1.21969				
vdsat	0.0975963	0.0975963	0.0931265				

• What is the CM level at the OTA output? Why?

$V_{ocm} = 0.874$ V The OTA output CM level settles at ~ 0.874 V because the CMFB loop forces the outputs to track the reference voltage ($V_{ref} = 0.88$ V).

• What is the CM level at the OTA input? Why?

$V_{icm} = 0.874$ V ,The large feedback resistors create a DC path that forces the input common-mode level to equal the output's.

2) Differential closed-loop response:

- Use AC analysis (1Hz:10Gz, logarithmic, 10 points/decade).
- Plot VODIFF vs frequency

 


Figure 24 : VODIFF vs frequency

- Use Measures or cursors to calculate circuit parameters (DC gain, CL BW, CL GBW)

```
gain      = 1.998060e+00 at= 1.258925e+03
bw        = 8.472513e+06
ugf       = 1.639110e+07
gbw = 1.692859e+07
```

Figure 25 : Closed Loop Gain and BW and UGF and GBW from simulation (Actual CMFB)

3) Differential and CMFB loops stability (STB analysis):

- Run STB analysis (in addition to AC analysis 1Hz:10Gz, logarithmic, 10 points/decade) two times: first using the 0V source in the diff path, and second using the 0V source in the CM path.

 


Figure 26 : A closed-loop testbench for simulating the AC response and stability of the OTA with capacitive feedback.

- Plot loop gain in dB and phase vs frequency for the two simulations overlaid.

 


Figure 27 : loop gain in dB and phase vs frequency for diff path and CM path overlaid

```

diff1_lg = 6.025642e+01
diff1_gx = 7.584074e+06
diff1_pm = 8.926434e+01
-----
cm1_lg = 7.155297e+01
cm1_gx = 9.558142e+06
cm1_pm = 7.083427e+01
  
```

Figure 28 : PM for diff path and CM path.

- Compare GBW and PM of diff and CM loops. Comment.

Parameter	diff path	CM path
DC Gain	60.26 dB	71.45 dB
GBW / UGF	7.58 MHz	9.56 MHz
PM	89.26°	70.08°

Comment :

The design successfully makes the common-mode loop faster than the differential loop, which is a key requirement for high-performance fully-differential amplifiers, while ensuring both loops are independently stable with ample phase margin.

- Compare DC LG and GBW of the diff loop with those obtained from open-loop simulation.

Parameter	Loop Gain (LG)	Open loop
DC Gain	60.26 dB	69.88 dB
GBW	7.58 MHz	51.03 MHz

Comment :

LG decreased due to beta effect ($\approx 1/3$) so GBW and DC Gain decreased

The DC gain difference is expected due to the feedback factor, while the lower closed-loop GBW accurately reflects the extra capacitive loading from the feedback network itself.

PART 6: Closed Loop Simulation (Transient Analysis)

1) Differential and CMFB loops stability (transient analysis) + CL settling time: Differential input pulse

- Apply a differential input pulse (initial value = 0, pulse value = 100mV, delay = 1us, period = 2us, pulse width = 1us, rise = fall = 10ns). → `PULSE(0 100m 1u 10n 10n 1u 2u)`
- Run transient analysis for 3us with 10ns max step.

Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOCM overlaid in the same figure.

 


Figure 29 : VINP, VINN, VOUTP, VOUTN, and VOCM overlaid for DIFF input pulse

 


Figure 30 : Vocm and Vodiff overlaid for DIFF input pulse

- Do you notice any differential/CM ringing? Are both loops stable with adequate PM?

No there is no ringing in both loops differential/CM, yes the both are stable cause the $PM > 70$

But there is a small (**glitch**) overshoot at Vocm case the $PM_{CM} = 70.8$ is less than 76

- Calculate the 1% settling time and compare it to the required specification. If the specification is not satisfied, what design changes could be a possible solution?

$$\text{settling} = 9.65624\text{e-}08$$

The simulated 1% settling time is 96.56 ns. This value successfully meets the required design specification of ≤ 100 ns.

If not satisfied you can increase GBW \rightarrow increase gm or decrease CL

2) Differential and CMFB loops stability (transient analysis): CM input pulse

- Set differential input to zero and apply the same previous pulse at the balun CM input.
- Run transient analysis for 3us to test the fully differential capacitive amplifier stability.
- Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOCM overlaid in the same figure.

 


Figure 31 : VINP, VINN, VOUTP, VOUTN, and VOCM overlaid for CM input pulse

- Do you notice any differential/CM ringing? Are both loops stable with adequate PM?

No there is no ringing in both loops differential/CM, yes the both are stable cause the $PM > 70$

But there an small (**glitch**) overshoot at Vocm case the $PM_{CM} = 70.8$ is less than 76

3) Output swing:

- Apply a differential sinusoidal input with freq = 100kHz and amplitude = 150mV.
- Run transient analysis for three periods (30us) with 0.1us max time step.
- Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOCM overlaid in the same figure.

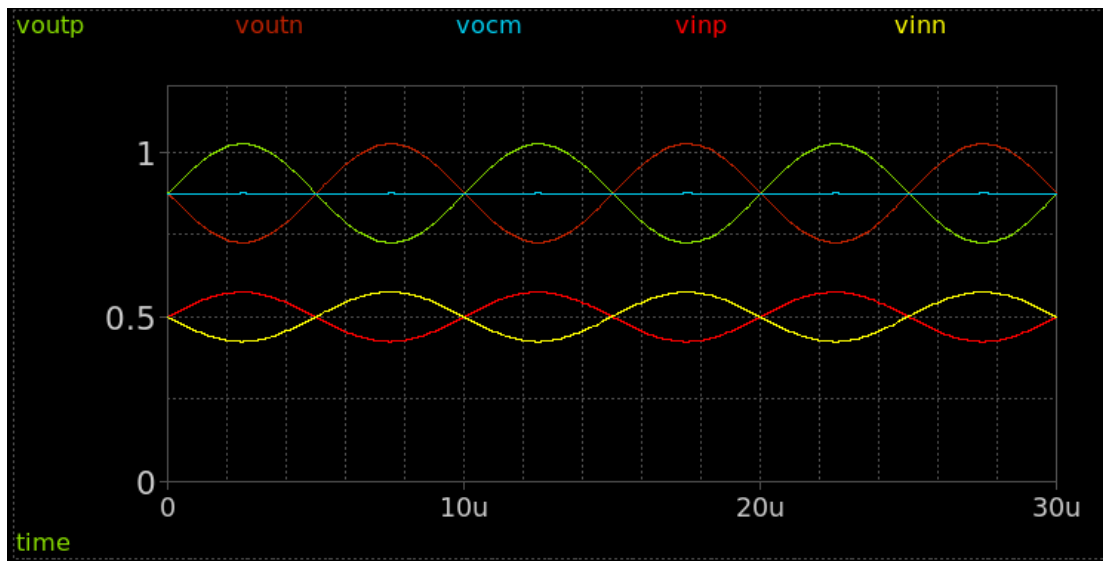


Figure 32 : VINP, VINN, VOUTP, VOUTN, and VOCM overlaid for differential sinusoidal input

- Plot the transient signals at VIDIFF and VODIFF overlaid in the same figure.

 


Figure 33 : VIDIFF and VODIFF overlaid for differential sinusoidal input

- Calculate the diff input and output peak-to-peak swings and the closed loop gain.

$$\text{Peak-to-peak} = 0.3 - (-0.3) = 0.6 \text{ V}$$

$$A_{ocl} = \frac{0.6 \text{ V}}{0.3 \text{ V}} = 2$$

Final Summary Folded-Cascode OTA Performance Verification :

Parameter	Specification	Simulated Result	Status
Closed-Loop Gain	2	1.998	✓
DC Loop Gain	≥ 60 dB	60.26 dB	✓
Phase Margin (PM)	$\geq 70^\circ$	89.26°	✓
Settling Time (1% error)	≤ 100 ns	96.56 ns	✓
Differential Output Swing	1.2 V _{pk-pk}	> 1.9 V (Available)	✓
CM Input Range – Low	≤ 0 V	-0.54 V	✓
CM Input Range – High	≥ 1 V	1.52 V	✓

Appendix

OP code

```
.control
save all
op
show m : id : gm : gds : vgs : vth : vds : vdsat
print allv
write lab11_OP.raw
.endc
```

Diff small signal

```
.control
save all
op
ac dec 10 1 10G
meas ac Gain MAX vmag(VOUT) FROM=1 TO=10G
let ff2=Gain*0.707
meas ac BW WHEN vmag(VOUT)=ff2 FALL =1
save v(VOUT)
remzerovec
write lab11_ac.raw
.endc
```

Loop gain"

```
.func tian_loop_1() {1/(1-1/(2*(ac1.l(v.X9999.Vi)*ac2.V(X9999.x)-
ac1.V(X9999.x)*ac2.l(v.X9999.Vi))+ac1.V(X9999.x)+ac2.l(v.X9999.Vi))))}
.func tian_loop_2() {1/(1-1/(2*(ac3.l(v.X9999.Vi1)*ac4.V(X9999.y)-
ac3.V(X9999.y)*ac4.l(v.X9999.Vi1))+ac3.V(X9999.y)+ac4.l(v.X9999.Vi1))))}
*-----
* Probes
*-----
.save V(X9999.x) l(v.X9999.Vi)
.save V(X9999.y) l(v.X9999.Vi1)
*-----
* CONTROL BLOCK
*-----
.control

set filetype=ascii
set num_threads=8
set color0=white
set color1=black
set xbrushwidth =3
unset askquit
```

```

optran 0 0 0 100n 4u 0
op
write stb.raw
set appendwrite
* -----
* First Loop STB analysis
* -----
* Set voltage AC to 1
alter i.X9999.li1 acmag=0
alter v.X9999.Vi1 acmag=0
alter v.X9999.Vi acmag=1
ac dec 50 100 10G
* Set Current to 1
alter i.X9999.li acmag=1
alter v.X9999.Vi acmag=0
ac dec 50 100 10G
* -----
* Second Loop STB analysis
* -----
* Set voltage AC to 1
alter i.X9999.li acmag=0
alter v.X9999.Vi acmag=0
alter v.X9999.Vi1 acmag=1
print loop1_LG
ac dec 50 100 10G
* Set Current to 1
alter i.X9999.li1 acmag=1
alter v.X9999.Vi1 acmag=0
ac dec 50 100 10G
let tian_signal_1 = tian_loop_1()
let loop_L1_gain_db = db(tian_signal_1)
let loop_L1_gain_ph = 180*cph(tian_signal_1)/pi
*plot loop_L1_gain_db
*plot loop_L1_gain_ph
save tian_signal_1
meas ac Gain_1 MAX vmag(tian_signal_1) FROM=1 TO=10G
let LG_L1 = 20*log10(Gain_1)
meas ac L1_GAIN_CROSSOVER_FREQ WHEN loop_L1_gain_db=0
meas ac L1_phaseatzerogain FIND loop_L1_gain_ph AT=L1_GAIN_CROSSOVER_FREQ
*let L1_PM = abs(180 - L1_phaseatzerogain)
*print L1_PM
let loop1_LG = LG_L1
let loop1_GX = L1_GAIN_CROSSOVER_FREQ
let loop1_PM = L1_phaseatzerogain
save loop1_LG
save loop1_GX
save loop1_PM

```

```

let tian_signal_2 = tian_loop_2()
let loop_L2_gain_db = db(tian_signal_2)
let loop_L2_gain_ph = 180*cph(tian_signal_2)/pi
*plot loop_L2_gain_db
*plot loop_L2_gain_ph
save tian_signal_2
meas ac Gain_2 MAX vmag(tian_signal_2) FROM=1 TO=10G
let LG_L2 = 20*log10(Gain_2)
meas ac L2_GAIN_CROSSOVER_FREQ WHEN loop_L2_gain_db=0
meas ac L2_phaseatzerogain FIND loop_L2_gain_ph AT=L2_GAIN_CROSSOVER_FREQ
*let L2_PM = abs(180 - L2_phaseatzerogain)
*print L2_PM
let loop2_LG = LG_L2
let loop2_GX = L2_GAIN_CROSSOVER_FREQ
let loop2_PM = L2_phaseatzerogain
save loop2_LG
save loop2_GX
save loop2_PM
let DIFF1_LG = loop1_LG
let DIFF1_GX = loop1_GX
let DIFF1_PM = loop1_PM
let CM1_LG = loop2_LG
let CM1_GX = loop2_GX
let CM1_PM = loop2_PM
echo -----
print DIFF1_LG DIFF1_GX DIFF1_PM
echo -----
print CM1_LG CM1_GX CM1_PM
echo -----
write Dstb.raw tian_signal_1 tian_signal_2
.meas ac CMGain MAX vmag(VODIFF) FROM=1 TO=1k
let ff2=Gain*0.707
.meas ac BW WHEN vmag(VODIFF)=ff2 FALL =1
let GBW      = Gain*BW
print GBW
.endc"

```

Settling time:

```
".control
save all
tran 10n 3u

let v_initial = x.
let v_final = x + margin
let v_swing = v_final - v_initial

let v_1_percent = v_initial + 0.01 * v_swing
let v_99_percent = v_initial + 0.99 * v_swing

meas tran t_ Settling TRIG v(VOUT) VAL=v_10_percent RISE=1 TARG v(VOUT) VAL=v_99_percent RISE=1

print t_ Settling

write Settling.raw
.endc"
```