



# **CMOS Analog IC Design**

## **Lab 1**

### **LPF Simulation and MOSFET Characteristics**

**Supervised by: Dr. Hesham Omran**

---

## PART 1: Low Pass Filter Simulation (LPF)

### Schematic :

Design a first order low pass filter that has  $R = 1k\Omega$  and 1ns time constant .

$T=RC$  then  $C=1p$

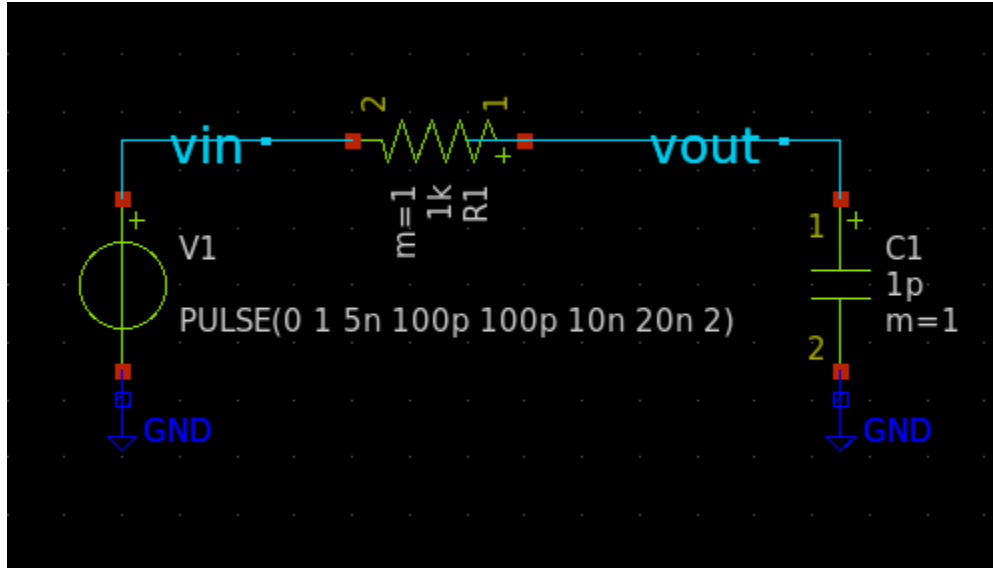


Figure 1 : first order low pass filter

### Transient Analysis :

Report transient analysis results for two periods

Code:

```
.control  
save all  
tran 100p 40n  
write rc_ckt.raw  
.endc
```

 


Figure 2 : Vin Vs Vout

Calculate rise and fall time (10% to 90%) using measure command. Export the results to an output text file.

Code:

```

"
.tran 100p 40n
.control
run
meas tran t_rise TRIG v(vout) VAL=0.1 RISE=1 TARG v(vout) VAL=0.9 RISE=1
meas tran t_fall TRIG v(vout) VAL=0.9 FALL=1 TARG v(vout) VAL=0.1 FALL=1
print t_rise > tran_result.txt
print t_fall >> tran_result.txt
.endc
.end
"

```

 


Figure 3 : T Rise &amp; Fall From the text file

Derive an analytical expression for the rise and fall times as a function of the RC time constant. Compare simulation with analytical results in a table.

## Analysis :

### Capacitor Calculation:

$$C = \frac{\text{Time Constant}}{R}$$

$$C = \frac{(1 * 10^{-9})}{1000} = 1 \text{ pF}$$

### Rise/Fall Time (10%-90%) Calculation:

$$t_{\text{rise}} = t_{\text{fall}} = \ln(9) * \text{Time Constant}$$

$$t_{\text{rise}} = t_{\text{fall}} = 2.197 * 1 \text{ ns}$$

$$t_{\text{rise}} = t_{\text{fall}} = 2.197 \text{ ns}$$

	Simulation	Analytical
Rise Time (ns)	2.195	2.197
Fall Time (ns)	2.196	2.197

Do parametric sweep for  $R = 1:1:5k\Omega$

Code:

```
.control
save all
let R_val = 1000
let R_stop = 5000
let R_step = 1000
while R_val le R_stop
alter R1 R_val
tran 100p 40n
meas tran t_rise TRIG v(vout) VAL=0.1 RISE=1 TARG v(vout) VAL=0.9 RISE=1
meas tran t_fall TRIG v(vout) VAL=0.9 FALL=1 TARG v(vout) VAL=0.1 FALL=1
print R_val t_rise >> tran_result.txt
print R_val t_fall >> tran_result.txt
write rc_ckt.raw
set appendwrite
let R_val = R_val + R_step
end
.endc
```

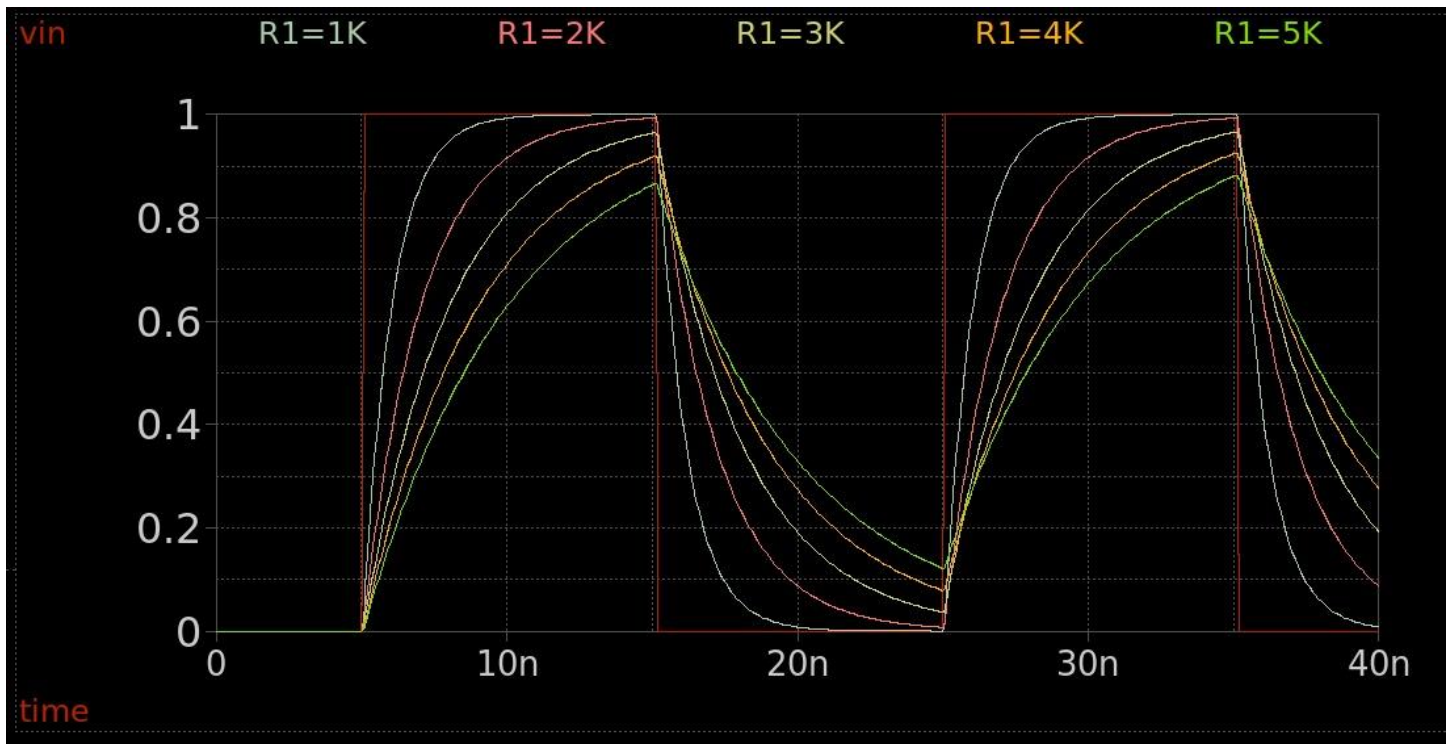


Figure 4 : Overlaid transient response from the parametric sweep for  $R = 1k\Omega$  to  $5k\Omega$

Comment :

- As the resistance  $R$  increases from  $1k\Omega$  to  $5k\Omega$ , the theoretical time constant  $\tau$  increases proportionally from  $1ns$  to  $5ns$ .
- The simulated rise time and fall time also increase approximately linearly, maintaining the same trend.

## AC Analysis :

### Schematic :

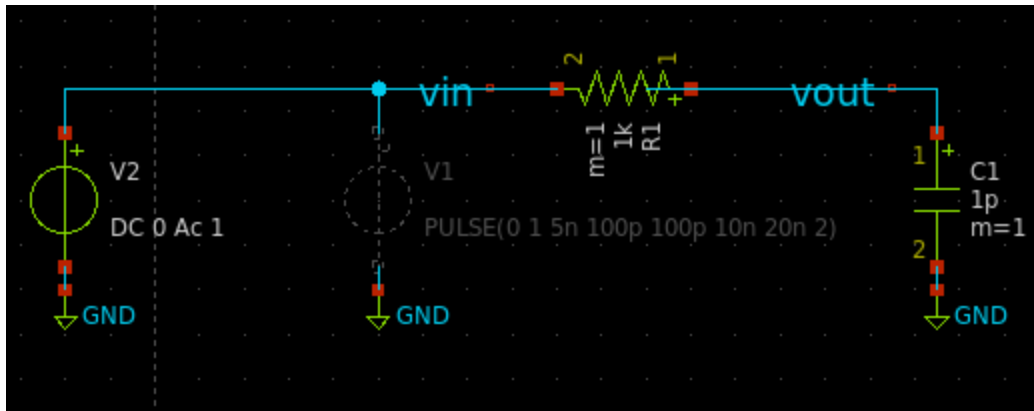


Figure 5 : Modify your testbench to perform ac analysis

Bode Plot (magnitude and phase) for the LPF

### Code:

```
.control
save all
ac dec 10 1 10g
write rc_ckt.raw
meas ac MAX_GAIN MAX vmag(vout) FROM=1 TO=10G
meas ac BW WHEN vmag(vout)=0.707 FALL=1
print MAX_GAIN BW >> ac_result.txt
.endc
```

 


Figure 6 : Bode Plot magnitude for LPF

 


Figure 7 : Bode Plot phase for LPF

Calculating DC gain and 3dB bandwidth and Export the results form text file .

 


Figure 8 : DC gain and 3dB bandwidth from text file

Derive an analytical expression (equation) for the bandwidth. Compare simulation with analytical results in a table.

### Analysis :

$$BW = f_{3dB} = \frac{1}{(2\pi RC)}$$

	Simulation	Analytical
<b>DC Gain (dB)</b>	<b>0</b>	<b>0</b>
<b>3dB Bandwidth (MHz)</b>	<b>159.25</b>	<b>159.15</b>

Do parametric sweep for R = 1,10,100,1000kΩ . Report overlaid results. Comment on the results

Code:

```
.control
save all
let R_val = 1k
let R_stop = 1meg
let R_mult = 10
while R_val le R_stop
alter R1 R_val
ac dec 10 1 10g
write rc_ckt.raw
set appendwrite
meas ac MAX_GAIN MAX vmag(vout) FROM=1 TO=10G
meas ac BW WHEN vmag(vout)=0.707 FALL=1
print R_val MAX_GAIN BW >> ac_result.txt
let R_val = R_val * R_mult
end
.endc
```



 


Figure 9 : Bode plot of the LPF showing the effect of sweeping the resistance


 


Figure 10 : phase of LPF showing the effect of sweeping the resistance

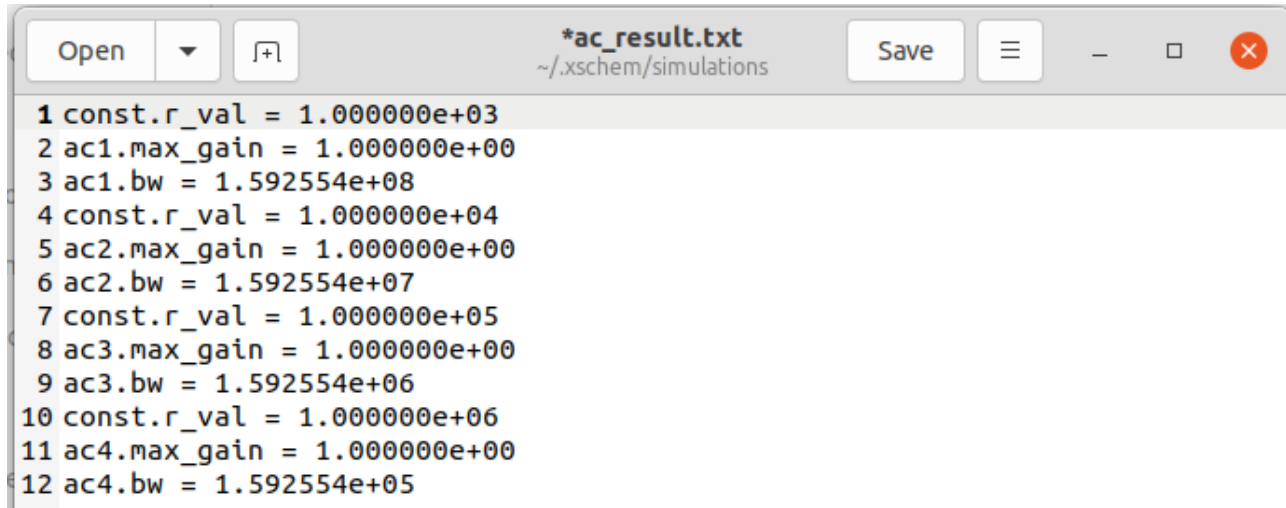

```
1 const.r_val = 1.000000e+03
2 ac1.max_gain = 1.000000e+00
3 ac1.bw = 1.592554e+08
4 const.r_val = 1.000000e+04
5 ac2.max_gain = 1.000000e+00
6 ac2.bw = 1.592554e+07
7 const.r_val = 1.000000e+05
8 ac3.max_gain = 1.000000e+00
9 ac3.bw = 1.592554e+06
10 const.r_val = 1.000000e+06
11 ac4.max_gain = 1.000000e+00
12 ac4.bw = 1.592554e+05
```

Figure 11 : Sweep Results: Resistance vs DC Gain & Bandwidth (from text file)

### Comment :

- As the resistance **R** increases, the filter's **cutoff frequency decreases**, meaning it starts blocking signals at lower frequencies.
- This relationship is inversely proportional: the data shows that when the resistance increases by a factor of 10, the bandwidth decreases by the same factor, while the passband gain remains constant at 0 dB.

## PART 2: MOSFET Characteristics

### Schematic :

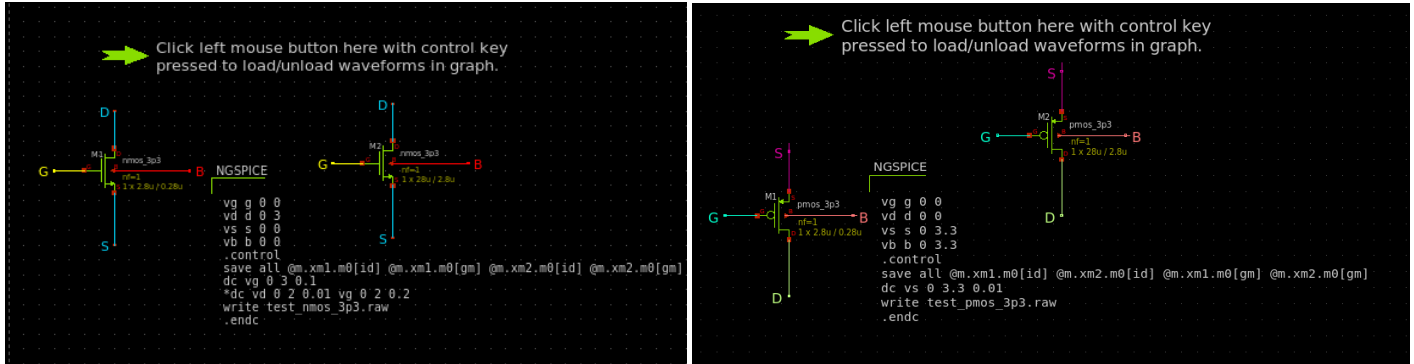


Figure 12 : Schematic & Code for NMOS and PMOS

For Short channel :  $W = 2.8\mu$  &  $L = 280n$

For Long channel :  $W = 28\mu$  &  $L = 2.8\mu$

Aspect ratio  $W/L = 10$  in both

### $I_D - V_{GS}$ characteristics for NMOS device :

 


Figure 13 : NMOS  $I_D$  vs  $V_{GS}$  &  $g_m$  vs  $V_{GS}$  for short and long channel.

## $ID - V_{GS}$ characteristics for PMOS device :

 


Figure 14 : PMOS  $ID$  vs  $V_{GS}$  &  $gm$  vs  $V_{GS}$  for short and long channel.

### Comment on the differences between short channel and long channel results.

- Which one has higher current? Why?

In Nmos Long channel have a higher current and in Pmos Short channel have a higher current why ? For NMOS, short-channel devices show lower current despite shorter  $L$  due to velocity saturation and mobility degradation. Long-channel follows the quadratic square-law, while short-channel exhibits a linear relation as secondary effects dominate .

For PMOS, short-channel devices have higher current despite velocity saturation and mobility degradation, because the reduced channel length dominates and short-channel effects are less severe compared to NMOS.

- Is the relation linear or quadratic? Why?

For long-channel, the relation is **quadratic** due to the square-law behavior of MOSFETs in saturation. For short-channel, it becomes **more linear** because high electric fields cause velocity saturation, breaking the square-law dependence.

## $I_D$ for NMOS & PMOS devices at $V_{GS} = V_{DD}$

 


Figure 15 :  $I_D$  For NMOS & PMOS at  $V_{GS} = V_{DD}$

For NMOS :

Id Short channel = 1.432 mA

Id Long channel = 3.216 mA

For PMOS :

Id Short channel = 0.6944 mA

Id Long channel = 0.7021 mA

### Comment on the differences between NMOS and PMOS.

- Which one has higher current? Why?

The NMOS transistor has a higher current. This is because the mobility of its charge carriers (electrons,  $\mu_n$ ) is significantly higher than the mobility of the PMOS charge carriers (holes,  $\mu_p$ ).

- What is the ratio between NMOS and PMOS currents at  $V_{GS} = V_{DD}$ ?

For Short channel:  $I_{D \text{ NMOS}} / I_{D \text{ PMOS}} = 4.6$

For Long channel:  $I_{D \text{ NMOS}} / I_{D \text{ PMOS}} = 2.1$

- Which one is more affected by short channel effects?

**NMOS is more affected by short-channel effects than PMOS** because electrons have higher mobility, making NMOS more prone to velocity saturation and mobility degradation.

## $g_m$ vs $V_{GS}$ using ADT :

For Short channel :  $W = 2.8\mu$  &  $L = 280\text{n}$

For Long channel :  $W = 28\mu$  &  $L = 2.8\mu$

Aspect ratio  $W/L = 10$  in both

For NMOS device :  $V_{DS} = V_{DD} = 3.3\text{V}$  &  $V_{GS} = 0 : 3.3$  &  $V_{SB} = 0$

 


Figure 16 :  $g_m$  vs  $V_{GS}$  in ADT

Comment on the differences between short channel and long channel results.

- Does  $g_m$  increase linearly? Why?


No, not perfectly. For the long-channel device, the increase is close to linear. For the short-channel device, the  $g_m$  begins to saturate at higher  $V_{GS}$  values. This is because  $g_m$  is the slope of the  $I_D$ - $V_{GS}$  curve, and effects like velocity saturation limit the current increase in short-channel devices.

- Does  $g_m$  saturate? Why?

Yes, the  $g_m$  of the short-channel device clearly saturates. This is a direct result of velocity saturation. When the charge carriers reach their maximum possible velocity, increasing  $V_{GS}$  further does not yield a proportional increase in current. As a result, the transconductance flattens out.
 
## ID vs VDS (use ADT)

For NMOS device :  $V_{DS} = 0:3.3$  &  $V_{GS} = 1:1:3$  &  $V_{SB} = 0$



**Comment on the differences between short channel and long channel results.**

- Which one has higher current? Why?

**In Nmos Long channel has a higher current** because short-channel devices show lower current despite shorter L due to velocity saturation and mobility degradation. Long-channel follows the quadratic square-law, while short-channel exhibits a linear relation as secondary effects dominate

- Which one has higher slope in the saturation region? Why?

**Short-channel devices have a higher slope** in the saturation region because they have a **lower output resistance  $r_o$**  due to stronger **channel length modulation** and **DIBL**, which degrade current saturation.

## $g_m$ and $r_o$ in Triode and Saturation (use ADT)

For NMOS device :  $V_{DS} = 0:3.3$  &  $V_{GS} = V_{th} + 0.5$  &  $V_{SB} = 0$

And  $V_{th} = 662\text{mV}$  from ADT then  $V_{GS} = 1.162\text{ V}$

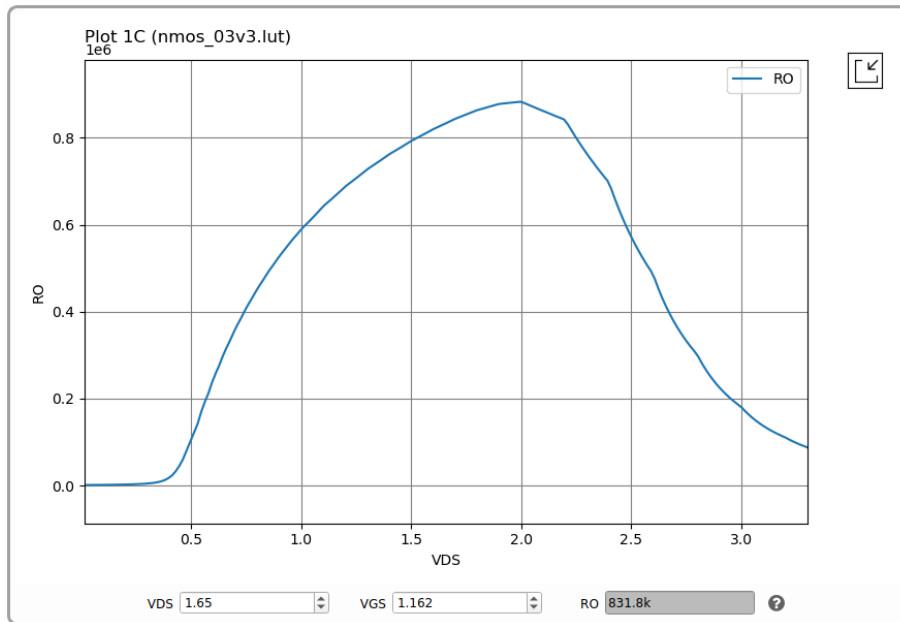


Figure 18 :  $r_o$  VS  $V_{DS}$  in ADT

### Comment

- In **short-channel MOSFETs**, as  $V_{DS}$  increases into deep saturation, **DIBL (Drain-Induced Barrier Lowering)** reduces the **threshold voltage  $V_{TH}$** , causing the **drain current** to rise more sharply. This increases the **slope of the  $I_D$  VS  $V_{DS}$  curve**, thereby reducing the **output resistance ( $r_o$ )**. So while  $r_o$  initially increases in saturation, it **eventually decreases at high  $V_{DS}$**  due to **DIBL**.



## Gm VS VDS

 


Figure 19 : Gm VS VDS in ADT

### Comment

- gm increases **linearly** in the **triode region** and becomes **constant** in **saturation**. This indicates that the **saturation region** provides a **stable** and **high transconductance**, which is **essential for analog amplifier design**